

Q1) $P = 30 \text{ Watt}$

$V = 120 \text{ V}$


$t = 1 \text{ min} = 60 \text{ s}$

$P = IV$

$I = \frac{P}{V} = \frac{30}{120} = 0.25$

$I = \frac{Q}{\Delta t} \Rightarrow Q = I \Delta t = 0.25 \times 60 = \underline{15 \text{ C}}$


Q2)

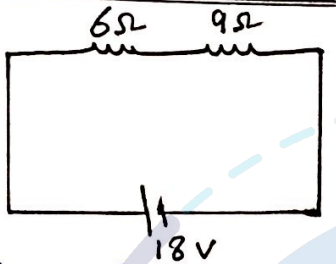

$R_T = 6 + 9 = 15 \Omega$

$\therefore I_T = \frac{18}{15} = 1.2$

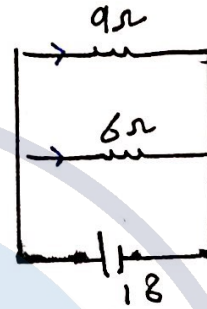$P_T = I^2 R_1 + I^2 R_2$
 $= (1.2)^2 (6) + (1.2)^2 (9)$
 $= \underline{21.6}$



$V_{6\Omega} = V_{9\Omega} = 18$

$\therefore P_T = \frac{V^2}{R_{9\Omega}} + \frac{V^2}{R_{6\Omega}}$

$P_T = \frac{(18)^2}{9} + \frac{(18)^2}{6} = 90$

$P = I V$
 $= \frac{V}{R} \cdot V$
 $P = \frac{V^2}{R}$

P_{max} سيكون في حالة التوزي لان الجهد لا يتوزع على المقاومين (متساوي في المقاومين).

Q3) $I = \frac{Q}{\Delta t} = \frac{Ne}{\Delta t}$
 $= \frac{5 \times 10^{21} \times 1.6 \times 10^{-19}}{10 \times 60} = 1.33$

$\therefore V = IR = 1.33 \times 20 = 26.66 \approx 27$

Q4) $R = \frac{\rho L}{A}$

$\frac{RA}{L} = \rho$

$\rho = \frac{0.45 \times (\pi (0.5 \times 10^{-3})^2)}{2} = 1.8 \times 10^{-7} \Omega \cdot m$

$$Q5) 137 = \frac{\rho}{\pi \left(\frac{D_{24}}{2}\right)^2} \sim ①$$

$$220 = \frac{\rho}{\pi \left(\frac{D_{26}}{2}\right)^2} \sim ②$$

بقسمة -
①
②

$$\sqrt{\frac{137}{220}} = \sqrt{\frac{(D_{26})^2}{(D_{24})^2}}$$

$$0.789 = \frac{D_{26}}{D_{24}} \Rightarrow \frac{D_{24}}{D_{26}} = \frac{1}{0.789} = 1.3$$

Q6) حجم الموصل يجب أن يبقى ثابتاً ، لذلك عند زيادة الطول تقل المساحة بحيث نحافظان على ثبات الحجم

$$\therefore V_{\text{الموصل}} = A L \uparrow$$

$$\therefore L_2 = 4 L_1$$

$$\therefore A_2 = \frac{1}{4} A_1$$

$$\left. \begin{array}{l} R_2 = \frac{\rho L_2}{A_2} \\ = \frac{\rho 4 L_1}{\frac{1}{4} A_1} = 16 \left(\frac{\rho L_1}{A_1} \right) \\ = 16 R_1 \end{array} \right\} \Rightarrow$$

Q9)


$$I = n e v_d A$$

$$|v_d| = \frac{I}{n e A}$$

$$|v_d| = \frac{1}{8.49 \times 10^{28} \times 1.6 \times 10^{-19} \times 0.4}$$

$$= 1.84 \times 10^{-10}$$

$$\vec{v}_d = -1.84 \times 10^{-10}$$

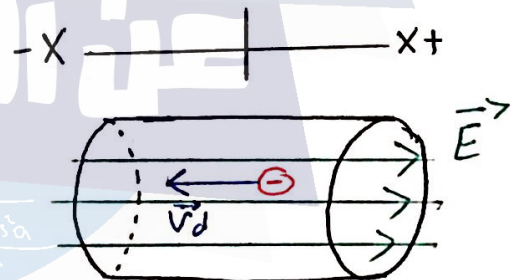

Q10) $R_{S_1} = 10 + 10 + 10 = 30 \Omega$


$R_p = \frac{30 \times 20}{30 + 20} = 12 \Omega$

$R_{S_2} = 5 + 12 = 17$

$I_T = \frac{11}{17} = 0.65 A$

$V_{5\Omega} = 0.65 \times 5 = 3.24$

$\therefore V_{20} = 11 - 3.24 = 7.8$

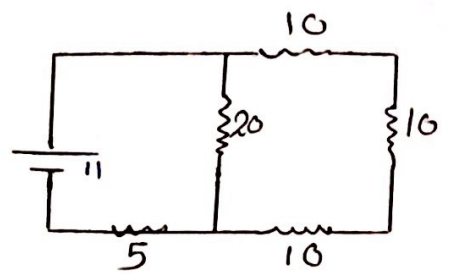

Q11) $R_{p_1} = \frac{10 \times 10}{10 + 10} = 5 \Omega$

$R_{S_1} = 5 + 5 = 10 \Omega$

$R_{p_2} = \frac{10 \times 10}{10 + 10} = 5 \Omega$

$R_{S_2} = 5 + 10 = 15 \Omega$



$I_T = \frac{24}{15} = 1.6$

$V_{10\Omega} = 10 \times 1.6 V$

$V_{10\Omega} = 8 V$
في التوازي

$I_{5\Omega} = \frac{1.6}{2} = 0.8$

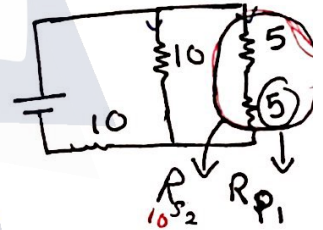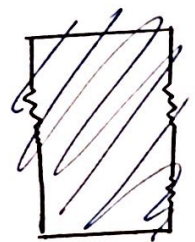$\therefore P_{5\Omega} = (0.8)^2 \times 5 = 3.2 \text{ Watt}$



هما أن المقاومتين متساويتان
إذا التيار سيتوزع بالتساوي
على المقاومتين في التوازي

Q12) $R_S = R_1 + R_2$

$R_{Total} = \frac{V_T}{I_T} = \frac{20}{2} = 10 \Omega$

$10 = R_1 + R_2 \Rightarrow R_1 = 10 - R_2 \text{ --- ①}$

$R_p = \frac{R_1 R_2}{R_1 + R_2}$

$R_T = \frac{20}{10} = 2 \Omega$

$\therefore 2 = \frac{R_1 R_2}{R_1 + R_2}$

$2R_1 + 2R_2 = R_1 R_2 \text{ --- ②}$

بالقويض في ② عن R_1

$2(10 - R_2) + 2R_2 = (10 - R_2)R_2$

$20 - 2R_2 + 2R_2 = 10R_2 - R_2^2$

$R_2^2 - 10R_2 + 20 = 0$

$R_2 = 7.23 \checkmark$

$R_1 = 2.8$

$$Q13) R_T = \frac{20}{2} = 10 \Omega$$

$$\therefore R_T < 15$$

∴ التوصل Parallel

$$10 = \frac{15R}{15+R}$$

$$15+R = 1.5R$$

$$15 = 0.5R$$

$$\therefore R = 30 \Omega$$

$$Q14) \therefore R_1 = R_2$$

$$\therefore I_{R_1} = I_{R_2} = 0.5$$


$$\therefore I_T = 0.5 + 0.5 = 1A$$

$$V_{R_1} = V_{R_2} \text{ (ولت التوصل توازي)}$$

$$\therefore V_{R_1} = 0.5 \times 24 = 12V = V_{R_2}$$

$$V_{R_3} = 1 \times 12 = 12V$$
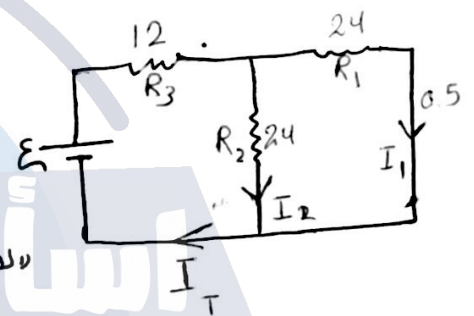
$$\therefore \mathcal{E} = 12 + 12 = 24V$$



$$Q15) I = I_1 + I_2 \Rightarrow I - I_1 - I_2 = 0 \quad \text{--- (3)}$$

$$10 - 5I_1 + 5I_2 = 0$$

$$5I_1 - 5I_2 = 10 \quad \text{--- (1)}$$

$$15 - 5I - 5I_2 = 0$$


$$5I + 5I_2 = 15 \quad \text{--- (2)}$$

بحل المعادلات ①، ②، ③ يندرج

$$I = 2.66$$

$$I_1 = 2.33$$

$$I_2 = 0.33$$

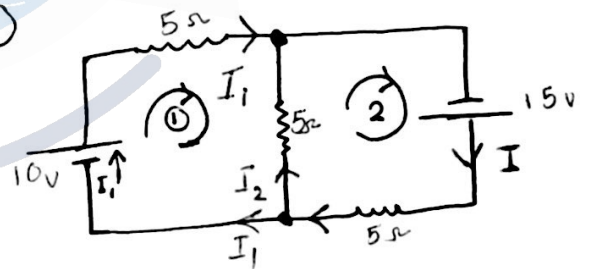


$$Q 16) 30 - 500I + 10 - 400 \times 30 \times 10^{-3} = 0$$

$$40 - 500I - 12 = 0$$

$$28 - 500I = 0$$

$$I = 0.056 = 56 \text{ mA}$$

from left to right

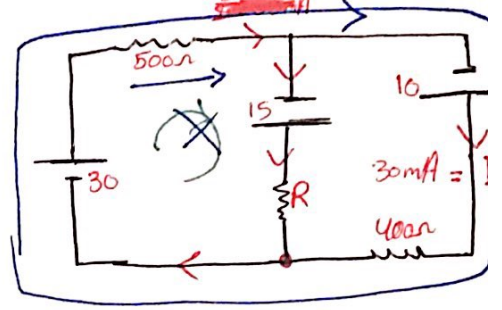

$$Q 17) 20 - 20 \times 1.5 - 12 = V_B - V_A$$

$$V_B - V_A = -22$$

$$Q 18) -30 - 6 + 12 - 10 + 4 = V_A - V_B$$

$$V_A - V_B = -30$$

$$Q 19) I = 0.4 + I_1 \Rightarrow I_1 = I - 0.4$$

$$10I + (0.4 \times 12) + 10I = V_A - V_B$$

$$20I + 4.8 = (V_A - V_B)$$

$$20I - (V_A - V_B) = -4.8 \quad \text{--- (1)}$$

$$10I + 8I_1 + 10I = (V_A - V_B)$$

$$20I + 8(I - 0.4) = (V_A - V_B)$$


$$20I + 8I - 3.2 = (V_A - V_B)$$

$$28I - (V_A - V_B) = 3.2 \quad \text{--- (2)}$$

بحل (1), (2) نتج

$$I = 1$$
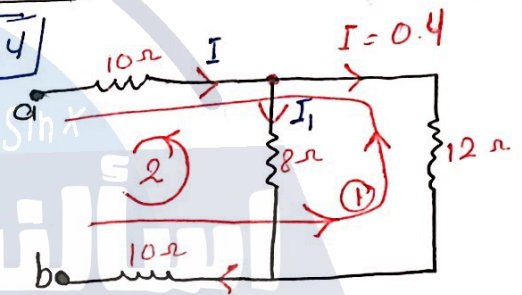
$$(V_A - V_B) = 24.8 \approx 25 \text{ V}$$



Q 20) $Q = Q_f (1 - e^{-t/\tau})$

$\frac{Q}{C} = \frac{Q_f}{C} (1 - e^{-t/\tau})$

$\mathcal{E} = \mathcal{E}_f (1 - e^{-t/\tau})$

$0.8 \mathcal{E}_f = \mathcal{E}_f (1 - e^{-t/\tau})$

$1.2 = \cancel{\mathcal{E}_f} e^{-t/\tau}$ « الطرفین ln »

$\cancel{1.2} = \cancel{\mathcal{E}_f} \frac{t}{\tau}$

$t = 1.6 \tau$

Q 21) $U = \frac{1}{2} C V_0^2$ ← الأصل

$0.45 U = \frac{1}{2} C V^2$
اطبقية

$0.45 (\frac{1}{2} C V_0^2) = \frac{1}{2} C V^2$

$0.45 V_0^2 = V^2$

$\sqrt{\frac{V^2}{V_0^2}} = \sqrt{0.45}$

$\frac{V}{V_0} = 0.67$ ①

$V = V_0 e^{-t/\tau}$
 $\frac{V}{V_0} = e^{-t/\tau}$ ②

$0.67 = e^{-t/\tau}$ « الطرفین ln »

$1.40 = \cancel{1} \frac{t}{\tau}$

$t = 0.4 \tau$

حل آخر

$U = U_0 e^{-\frac{2t}{\tau}}$ باستخدام القانون

$0.45 U_0 = U_0 e^{-\frac{2t}{\tau}}$

$\ln 0.45 = \ln e^{-\frac{2t}{\tau}}$

$\cancel{-0.8} = \cancel{1} \frac{2t}{\tau}$

$t = \frac{0.8}{2} \tau \Rightarrow t = 0.4 \tau$

$$Q_{22}) Q_f = 30 \times 30 = 900 \mu C$$

$$Q = Q_f (1 - e^{-t/\tau})$$

$$Q = 900 (1 - e^{-t/\tau}) \quad \text{--- (1)}$$

~~$V = 30 \times 10^{-3} \times 1000 \times 10^{-6}$~~

$$\tau = (5 \times 10^{-3}) (30 \times 10^{-6}) = 0.15$$

$$I_{max} = \frac{30}{5 \times 10^{-3}} = 6 \times 10^{-3} A = 6 mA$$

$$I = I_{max} e^{-t/\tau}$$

$$2 = 6 e^{-t/0.15}$$

$$\frac{1}{3} = e^{-t/0.15} \quad \text{« الطرفين ln »}$$

$$1.1 = \frac{t}{0.15}$$

$$t = 0.165 s$$

$$\therefore Q = 900 (1 - e^{-\frac{0.165}{0.15}})$$

$$Q = 600 \mu C$$

$$V_{capacitor} = \frac{600 \times 10^{-6}}{30 \times 10^{-6}} = 20 V$$

$$\therefore P_{(rate)} = I V$$

$$= (2 \times 10^{-3}) (20) = 40 \times 10^{-3} Watt = 40 mWatt$$

Q23) $Q_f = 40 \times 50 = 2000 \mu C$

$\tau = (40 \times 10^{-6})(5 \times 10^3) = 0.2$

$I_{max} = \frac{50}{5 \times 10^3} = 10 \times 10^{-3} = 10 \text{ mA}$

$I = I_{max} e^{-\frac{t}{\tau}}$

$2 = 10 e^{-\frac{t}{0.2}}$

$\frac{1}{5} = e^{-\frac{t}{0.2}}$

$1.61 = \frac{t}{0.2}$

$t = 0.32$

$Q = 2000 (1 - e^{-\frac{0.32}{0.2}})$
 $= 1596.21 \mu C$

$U = \frac{1}{2} \frac{Q^2}{C}$
 $= \frac{1}{2} \times \frac{(1596.21 \times 10^{-6})^2}{40 \times 10^{-6}} = 0.032 \text{ J} = 32 \text{ mJ}$

Q24) $R_{p1} = \frac{30 \times 30}{30 + 30} = 15$

$R_{s1} = 30 + 15 = 45$

$R_{p2} = \frac{30 \times 45}{30 + 45} = 18$




Q25) $R_{s1} = 12 + 12 = 24$

$R_{s2} = 12 + 12 = 24$

$R_{p1} = \frac{24 \times 12}{24 + 12} = 8$

$R_{p2} = \frac{24 \times 12}{24 + 12} = 8$

$R_{s3} = 8 + 8 = 16$

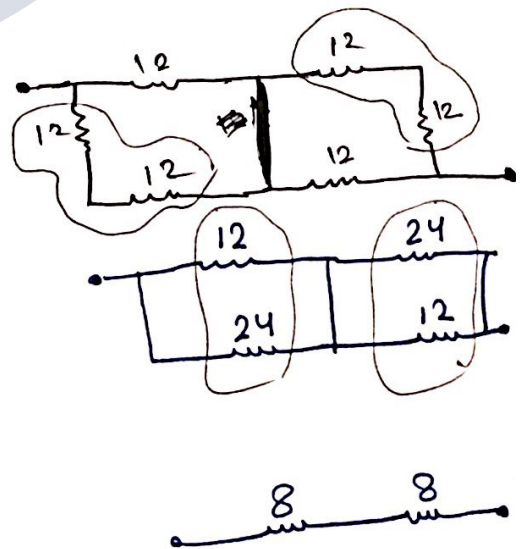


$$Q_{24}) R_{p_1} = \frac{80 \times 80}{80 + 80} = 40 \Omega$$

$$R_{p_2} = \frac{40 \times 40}{40 + 40} = 20 \Omega$$

$$R_{p_3} = \frac{20 \times 20}{20 + 20} = 10 \Omega$$

$$R_S = 10 + 20 + 30 \\ = 70 \Omega$$

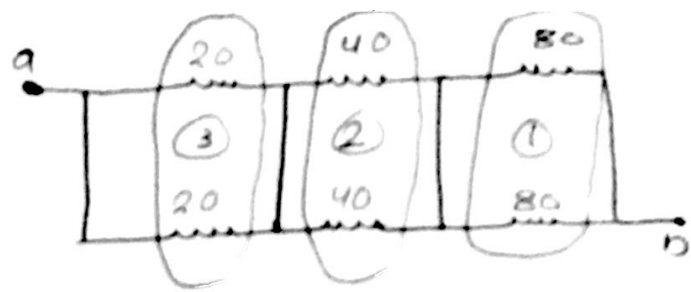

Ch 27

1) $|\vec{B}| = \sqrt{2^2 + 3^2 + (-4)^2} = 5.4 \text{ mT}$

$\vec{F}_B = q \vec{v} \times \vec{B}$

$= q v B \sin \theta$

$= (5 \times 10^9)(5 \times 10^3)(5.4 \times 10^{-3}) \sin 120$

$= 1.17 \times 10^{-7} \text{ N}$

$F = ma$


$1.17 \times 10^{-7} = 3 \times 10^{-9} \times a$

$a = 38.9 \approx 39 \text{ m/s}^2$

$\mu g = 10^{-6} \text{ g}$

$= 10^{-9} \text{ Kg}$

4)

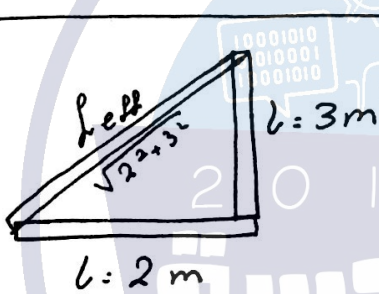


$F_B = I \vec{l}_{eff} \times \vec{B}$

$= 25 \times \sqrt{2^2 + 3^2} \times (40 \times 10^{-3}) \sin 90$

$= 3.60 \text{ N}$

6)

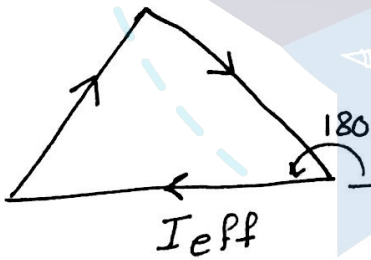

$\vec{F} = I \vec{l}_{eff} \times \vec{B}$

$= I \times l \times B \sin 180$

$\rightarrow B = \text{Zero}$

7) $\vec{\mu} = I \vec{A}$

$\mu = NI A$

$= 80 \times (8) \times (0.4 \times 0.3)$


$= 76.8$

$\tau = \vec{\mu} \times \vec{B}$

$= \mu B \sin \theta$

$= 76.8 \times (40 \times 10^{-3}) \sin 60$

$= 2.66 \approx 2.7 \text{ N.m}$

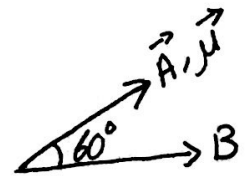

$$8) 80 = 2\pi r$$

$$r = 12.7 \text{ cm} = 0.127 \text{ m}$$

$$A = \pi (0.127)^2$$


$$= 0.051 \text{ m}^2$$

$$\tau = \vec{\mu} \times \vec{B}$$

$$\tau = I \vec{A} \times \vec{B}$$

$$= IAB \sin \theta$$
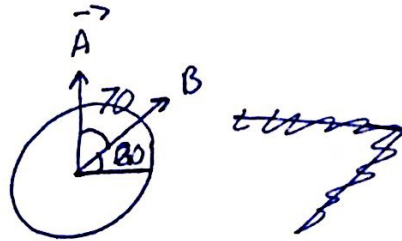
$$= 4 \times 0.051 \times 2 \times \sin 70 = \underline{0.38 \text{ N.m}}$$



$$9) \tau = \vec{\mu} \times \vec{B}$$

$$= I \vec{A} \times \vec{B}$$

$$\vec{A} = A \hat{n} = (\pi (0.5)^2) \frac{(2\hat{i} - \hat{j} + 2\hat{k})}{3}$$

normal
vector

$$= 0.26 (2\hat{i} - \hat{j} + 2\hat{k})$$

$$\vec{A} = 0.52\hat{i} - 0.26\hat{j} + 0.52\hat{k}$$

$$\vec{A} \times \vec{B} = \begin{vmatrix} \hat{i} & \hat{j} & \hat{k} \\ 0.52 & -0.26 & 0.52 \\ 2 & -6 & 0 \end{vmatrix}$$

$$\vec{A} \times \vec{B} = [0.26 \quad 0.52] \hat{i} - [\quad] \hat{j} - [\quad] \hat{k}$$

$$= (-0.26 \times 0 - (-6 \times 0.52)) \hat{i}$$

$$\vec{A} \times \vec{B} = 3.12 \hat{i}$$

$$\tau_x = I \vec{A} \times \vec{B}_x$$

$$= 3 \times 3.12$$

$$= 9.36 \approx 9.4$$

$$110) \vec{\mu} = I \vec{A}$$


$$= NI \vec{A}$$

$$= 50 \times 0.5 \times (0.2)^2 = 1$$

$$\tau = \vec{\mu} \times \vec{B}$$

$$= \mu B \sin \theta$$

$$= 1 \times 0.4 \sin 60 = 0.35$$

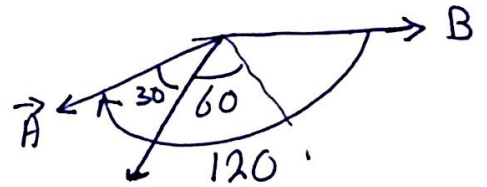

$$11) \tau = IN \vec{A} \times \vec{B}$$

$$\tau = INAB \sin \theta \leftarrow 90$$

$$0.080 = I \times 200 \times (0.2 \times 0.8) \times 0.3$$

$$0.080 = 9.6 I$$

$$I = 8.3 \times 10^{-3} \text{ A} = 8.3 \text{ mA}$$

$$12) \rho = V_{\parallel} \text{ (T)}$$

$$\rho = V_{\parallel} \times \frac{2\pi}{\omega}$$

$$\rho = V_{\parallel} \times \frac{2\pi r}{V_{\perp}}$$

$$r = \frac{m V_{\perp}}{B q}$$

$$V_{\perp} = \frac{B q r}{m}$$

$$V_{\perp} = \frac{(80 \times 10^{-6})(1.6 \times 10^{-19})(2 \times 10^{-3})}{(9.11 \times 10^{-31})}$$

$$V_{\perp} = 28.1 \text{ Km/s}$$

$$V_{\parallel} = \frac{\rho}{T} = \frac{(9 \times 10^{-3})}{\frac{2\pi (2 \times 10^{-3})}{28.1 \times 10^3}} = 20.1 \text{ Km/s}$$

$$V = \sqrt{V_{\parallel}^2 + V_{\perp}^2}$$

$$= \sqrt{(28.1)^2 + (20.1)^2}$$

$$= 34.5 \approx 35 \text{ Km/s}$$

$$13) F_B = F_c$$

$$q v_{\perp} B = \frac{m v_{\perp}^2}{r}$$

$$\omega = \frac{qB}{m} \Rightarrow T = \frac{2\pi}{\omega} \Rightarrow \boxed{T = \frac{2\pi m}{qB}}$$

$$T = \frac{2\pi (1.67 \times 10^{-27})}{(1.6 \times 10^{-19})(0.5)} = 1.3 \times 10^{-7} \text{ s}$$

$$\rho = v_{\perp} T$$

$$\rho = v \cos \theta T$$

$$5 \times 10^{-3} = (60 \times 10^3) \cos \theta \times 1.3 \times 10^{-7}$$

$$5 \times 10^{-3} = 8 \times 10^{-3} \cos \theta$$

$$\cos \theta = \frac{5}{8} \Rightarrow \boxed{\theta = 51^\circ}$$

$$14) \rho = v_{\parallel} \times \frac{2\pi r}{v_{\perp}}$$

$$\rho = v \cos \theta \times \frac{2\pi r}{v \sin \theta} \Rightarrow \rho = \frac{2\pi r}{\tan \theta}$$

$$\tan \theta = \frac{2\pi (4 \times 10^{-2})}{(8 \times 10^{-2})^2}$$

$$\tan \theta = \pi$$

$$\boxed{\theta = 72^\circ}$$

~~$$\rho = \tan \theta \times 2\pi r$$

$$\frac{2 \times 8 \times 10^{-2}}{2\pi (4 \times 10^{-2})} = \tan \theta$$

$$\tan \theta = \frac{2}{\pi}$$~~

15) \vec{B} uniform
 v isn't $\perp B$ \Rightarrow helical

$$r = \frac{m v}{q B} = \frac{3 \times 10^{-9} \times 40 \times 10^3}{5 \times 10^{-6} \times 60 \times 10^3} = 0.4 \text{ m} = 40 \text{ cm}$$

$$\rho = 30 \times \frac{2\pi \times 0.4}{60} = 1.3 \text{ m}$$

16) $KE = U_e$

$$\frac{1}{2} m v^2 = e V$$

$$v = \sqrt{\frac{2 e V}{m}}$$

$$r = \frac{m v}{q B}$$

جواب

$$\frac{r_1}{r_2} = \frac{V_1}{V_2}$$

$$\frac{r_1}{r_2} = \frac{\sqrt{\frac{2 e V_1}{m}}}{\sqrt{\frac{2 e V_2}{m}}}$$

$$\frac{r_1}{r_2} = \frac{\sqrt{500}}{\sqrt{300}} = 1.29 \approx 1.3$$

17) $r = \frac{m v}{q B}$

$$2 \times 10^{-3} = \frac{(1.67 \times 10^{-27}) v \sin 45^\circ}{(1.6 \times 10^{-19}) (0.25)}$$

$$v = 48 \times 10^3 \text{ m/s} = \underline{48 \text{ Km/s}}$$

$$\therefore d = 48 \times 1 = 48 \text{ Km}$$

18) ~~max~~

$$r_2 - r_1 = (2.5 \times 10^{-2})$$

$$\frac{m_2 v}{qB} - \frac{m_1 v}{qB} = (2.5 \times 10^{-2})$$

$$\frac{v}{qB} (m_2 - m_1) = (2.5 \times 10^{-2})$$

$$(m_2 - m_1) = \frac{(2.5 \times 10^{-2}) qB}{v}$$

$$(m_2 - m_1) = \frac{(2.5 \times 10^{-2}) (1.6 \times 10^{-19}) (0.4)}{5000 \times 10^3} = 3.2 \times 10^{-28} \text{ Kg}$$

19) $F_B = F_e$

$$qvB = qE$$

$$v = \frac{E}{B}$$

$$v = \frac{4 \times 10^3}{8 \times 10^{-3}} = 500 \times 10^3$$

$$KE = \frac{1}{2} m v^2$$

$$= \frac{1}{2} (9.11 \times 10^{-31}) (500 \times 10^3)^2$$

$$= \frac{1.14 \times 10^{-19}}{1.6 \times 10^{-19}} \text{ J}$$


$$\approx 0.71 \text{ eV}$$

للتحويل من J إلى eV
نقسم على شحنة الإلكترون
 1.6×10^{-19}

$$Q9) B_{\text{wire}} = \frac{\mu_0 \times 40}{2\pi(0.2)} = 4 \times 10^{-5} \Rightarrow 40 \mu T$$

$$B_{\text{ext}} = 30 \mu T$$
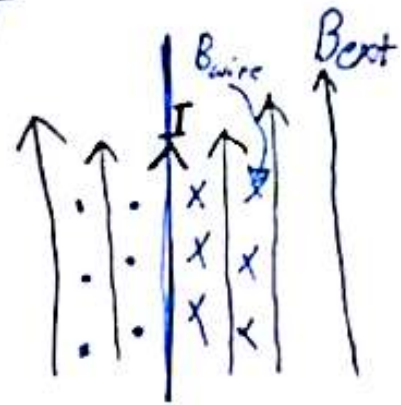
$$B_{\text{total}} = \sqrt{(40)^2 + (30)^2} = 50 \mu T$$




المجالين متعامدين


$$Q8) B_1 = \frac{\mu_0 \times 60}{2\pi(2 \times 10^{-3})} = 6 \times 10^{-3} \odot$$

$$B_2 = \frac{\mu_0 (60)}{2\pi(3 \times 10^{-3})} = 4 \times 10^{-3} \odot$$
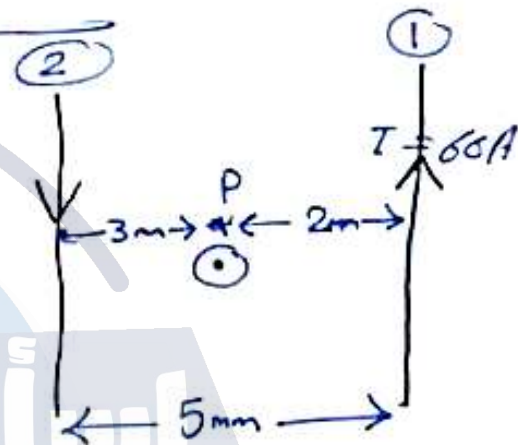
$$B_{\text{at } p} = (6 + 4) \times 10^{-3} = 10 \times 10^{-3} = 10 \text{ mT}$$



Q6)

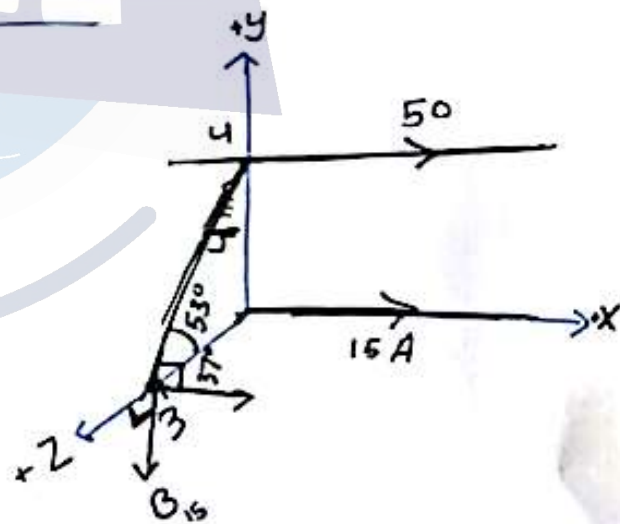

$$Q12) \theta = 90 \times \frac{\pi}{180} = \boxed{\frac{\pi}{2}}$$

نفس فكرة 13

$$Q11) L = (2\pi r) N$$

$$x = 2\pi r \times 5$$

$$r = 0.064 \text{ m}$$

$$B = \frac{\mu_0 \times 5 \times 1.2}{2 \times 0.064} = 5.9 \times 10^{-5} = 59 \mu\text{T}$$

$$Q10) \frac{I_1}{I_2} = \frac{3}{1} \Rightarrow I_1 = 3I_2$$

$$B_{\text{total}} = B_1 + B_2$$


$$4 \times 10^{-6} = \frac{\mu_0 I_1}{2\pi(0.1)} + \frac{\mu_0 I_2}{2\pi(0.1)}$$

$$4 \times 10^{-6} = \frac{\mu_0}{2\pi(0.1)} [3I_2 + I_2]$$

$$4 \times 10^{-6} = \frac{\mu_0 \times 4I_2}{2\pi(0.1)}$$

$$I_2 = 0.5 \text{ A}$$

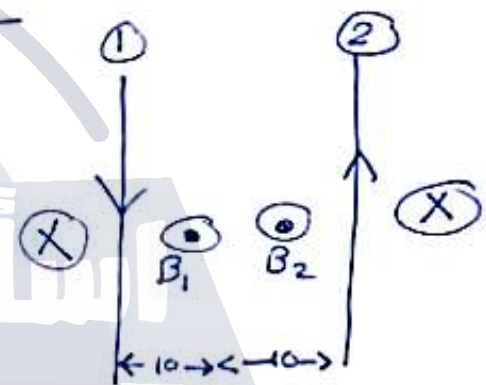
$$I_1 = 3 \times 0.5 = 1.5 \text{ A the largest}$$



Q15)

$$\Sigma F = 2 \times \frac{\mu_0 \times 10^2 \times (0.2) \times \cos 30}{2\pi(0.1)}$$

$$= 69 \mu N$$

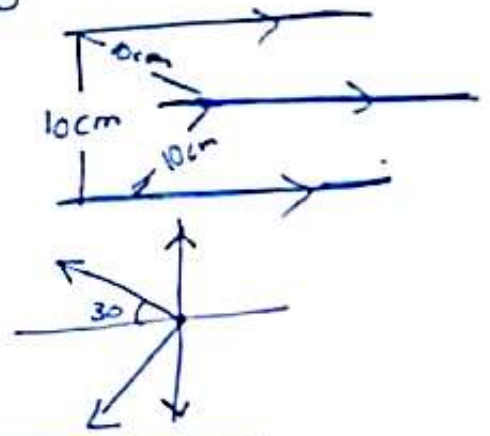

Q14)

$$B_a = \frac{\mu_0 I \odot}{4\pi a} \rightarrow \frac{270 \times \pi}{180} = \boxed{\frac{3\pi}{2}}$$

$$B_a = \frac{\mu_0 I \left(\frac{3\pi}{2}\right)}{4\pi R} = \boxed{\frac{3\mu_0 I}{8R}} \odot$$

$$B_b = \frac{\mu_0 I \left(\frac{3\pi}{2}\right)}{4\pi(2R)} = \boxed{\frac{3\mu_0 I}{16R}} \otimes$$

$$B = \frac{3\mu_0 I}{8R} - \frac{3\mu_0 I}{16R} = \boxed{\frac{3\mu_0 I}{16R}}$$

Q13)

$$B_a = \frac{\mu_0 \times 5 \times 2\pi}{4\pi(0.02)} = 1.57 \times 10^{-4} \otimes$$

$$\odot = \frac{360 \times \pi}{180} = 2\pi$$

$$B_b = 6.98 \times 10^{-5} \odot$$

$$B = 1.57 \times 10^{-4} - 6.98 \times 10^{-5} = 8.7 \times 10^{-5} \otimes$$


$$87 \mu T$$

$$Q18) F_{\text{result}} = F_{AC} \sin 30 + F_{AB} \sin 30$$

$$= (0.032 \sin 30) \times 2$$

$$= 0.032$$

$$= 32 \text{ mN}$$

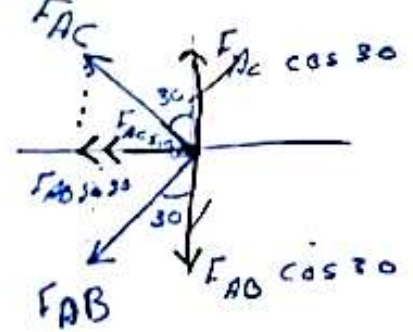


$$F_{AC} = \frac{\mu_0 (20)^2 (2)}{2\pi (5 \times 10^{-3})}$$

$$= 0.032 \text{ N} = F_{AB}$$

Q17)




نفس
الضوء

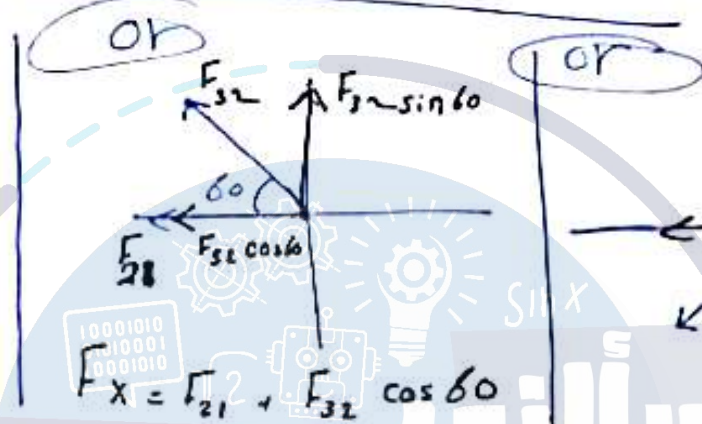


$$F_y = F_{32} \sin 60$$

$$\Sigma F = \sqrt{F_x^2 + F_y^2}$$

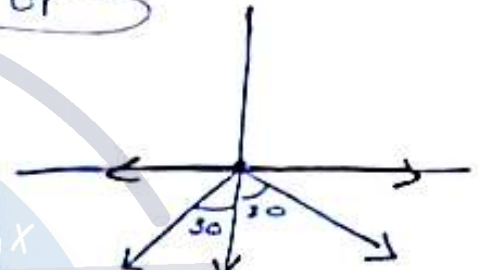

$$F = 2 \cos(30)$$

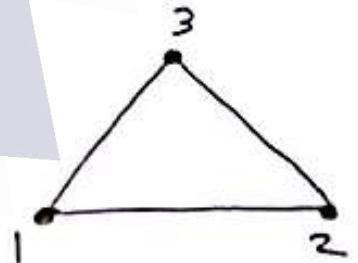

Q16)

$$I_1 = 3I_2$$

$$F = \frac{\mu_0 I_1 I_2 L}{2\pi r}$$

$$60 \times 10^{-6} = \frac{\mu_0 (3I_2) I_2 (2)}{2\pi (0.02)}$$

$$I_2^2 = 1 \Rightarrow I_2 = 1 \text{ A}$$


$$\therefore I_1 = 3 \text{ A} \checkmark$$

the greatest



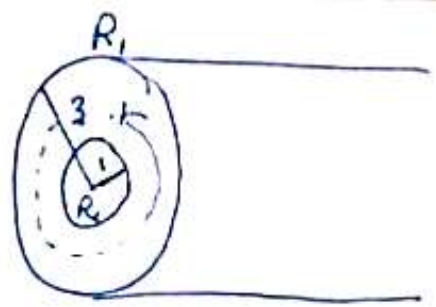Q21)

$$B = \frac{\mu_0 I (r^2 - R_2^2)}{(2\pi r) (R_1^2 - R_2^2)}$$




$$= \frac{\mu_0 \times 80 \times ((2 \times 10^{-3})^2 - (1 \times 10^{-3})^2)}{2\pi (2 \times 10^{-3}) ((3 \times 10^{-3})^2 - (1 \times 10^{-3})^2)}$$

$$= 3 \text{ mT}$$

Q20) $r > 1 \text{ mm}$

$$B = \frac{\mu_0 I}{2\pi r}$$

تحويل
مباشر

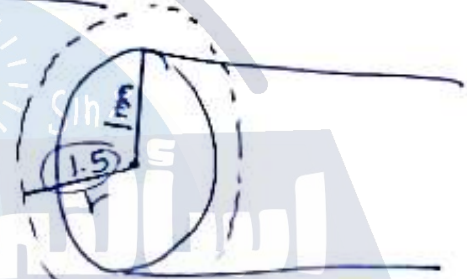

Q18) $F_x = F_{BC} \cos 60 + F_{AC} \cos 60$

كفوى التيار ←


$$= \frac{\mu_0 (20)^2 \times 2}{2\pi (5 \times 10^{-3})} + \frac{\mu_0 (20)^2 (2)}{2\pi (5 \times 10^{-3})} \cos 60$$

$$= 0.032 + 0.016 = 0.048 \text{ N}$$

$$F_y = F_{AC} \sin 60$$

$$= 0.028 \text{ N}$$

$$F = \sqrt{(0.028)^2 + (0.048)^2}$$

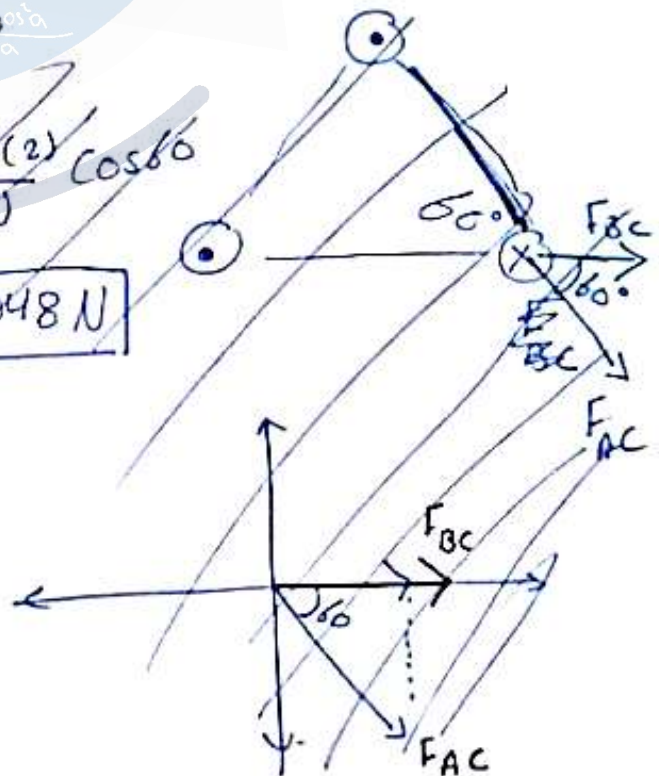

Q 23)

$$B(2\pi r) = \mu_0 I_{inc}$$

$$B(2\pi r) = \mu_0 \frac{I A_{المقطع}}{A_{الكلي}}$$

$$B(2\pi r) = \mu_0 I \frac{\pi(r^2 - R_2^2)}{\pi(R_1^2 - R_2^2)}$$


$$B_{cylindrical conductor} = \frac{\mu_0 I (r^2 - R_2^2)}{(2\pi r)(R_1^2 - R_2^2)}$$

$$= \frac{\mu_0 \times 24 \times ((3 \times 10^{-3})^2 - (2 \times 10^{-3})^2)}{2\pi (3 \times 10^{-3}) ((4 \times 10^{-3})^2 - (2 \times 10^{-3})^2)}$$

$$= 6.67 \times 10^{-4} \Rightarrow \boxed{0.667 \text{ mT}}$$

$$B_{wire} = \frac{\mu_0 \times 24}{2\pi (3 \times 10^{-3})} = 1.6 \times 10^{-3} = \boxed{1.6 \text{ mT}}$$

$$|B_{result}| = 1.6 - 0.667 = 0.93 \text{ mT}$$

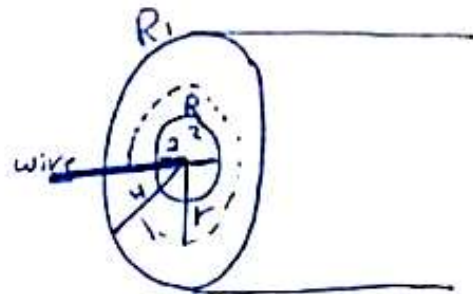

$$J = \frac{I}{A}$$

$$A_{الكلي}$$


$$A = \pi R_2^2 - \pi R_1^2$$

Q 22) $B(2\pi r) = \mu_0 I_{inc}$

$$B = \frac{\mu_0 I}{2\pi r}$$

$$= \frac{\mu_0 (24)}{2\pi (5 \times 10^{-3})} = 9.6 \times 10^{-4} \text{ T}$$

$$= 0.96 \text{ mT}$$

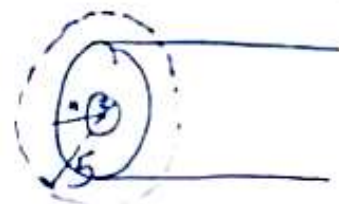

$$Q27) \quad \underset{\text{on wire}}{F} = \underset{\text{Solenoid}}{B} \underset{\text{wire}}{I} L$$

$$F = (\mu_0 n I) I L$$

$$= (\mu_0 \times 800 \times 50 \times 10^{-3}) (12) (0.02)$$

$$= 1.2 \times 10^{-5} \text{ N} = 12 \mu\text{N}$$

$$Q26) \quad n = \frac{8000}{2} = 2000$$

$$B = \mu_0 \times 2000 \times 5 = 0.0125 \text{ T}$$

$$\phi = \vec{B} \cdot \vec{A}$$

$$\phi = (0.0125) (\pi (0.02)^2) \cos 0$$

$$= 1.6 \times 10^{-5} \text{ Wb} = 16 \mu\text{Wb}$$

$$Q25) \quad B_{\text{sol}} = \mu_0 (900) (30 \times 10^{-3}) = 3.4 \times 10^{-5}$$

$$B_{\text{wire}} = \frac{\mu_0 (3)}{2\pi (0.02)} = 3 \times 10^{-5}$$

$$B_{\text{result}} = \sqrt{(3 \times 10^{-5})^2 + (3.4 \times 10^{-5})^2}$$

$$= 4.5 \times 10^{-5} \text{ T} = 45 \text{ mT}$$

Q 37)

$$B = \frac{\mu_0 N I}{2 \pi r}$$

$$= \frac{(4\pi \times 10^{-7}) (2000) (30)}{2 \pi (0.11)} = 0.109 \text{ T}$$

Q 30)

$$\oint B \cdot ds = \mu_0 (I_{enc})$$

$$= \mu_0 (J) (A_{\text{المطلوب}}) \Rightarrow (1.5 \times 10^{-2})^2 = 2.25 \times 10^{-4}$$

$$= \mu_0 I A_{\text{المطلوب}}$$

$$(3 \times 10^{-2})^2 = 9 \times 10^{-4}$$


$$= \frac{(4\pi \times 10^{-4}) (60) (2.25 \times 10^{-4})}{(9 \times 10^{-4})}$$

$$= 1.9 \times 10^{-5} \text{ T} = 19 \mu\text{T}$$

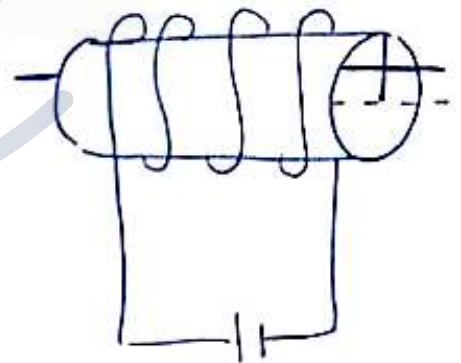Q 28) $B_{sol} = \mu_0 n I$

$$= \mu_0 (1200) (0.3) = 4.5 \times 10^{-4}$$

$$B_{wire} = \frac{\mu_0 (20)}{2 \pi (0.01)} = 4 \times 10^{-4}$$



المجال الناشئ في ال solenoid باتجاه $\pm X$
 المجال الناشئ عن ال wire (خارج وداخل الصفحة) $\pm Z$
 \therefore المجالين متعامدين

$$B_{result} = \sqrt{(4 \times 10^{-4})^2 + (4.5 \times 10^{-4})^2}$$

$$= 6.0 \times 10^{-4} \text{ T}$$

$$= 0.60 \text{ mT}$$