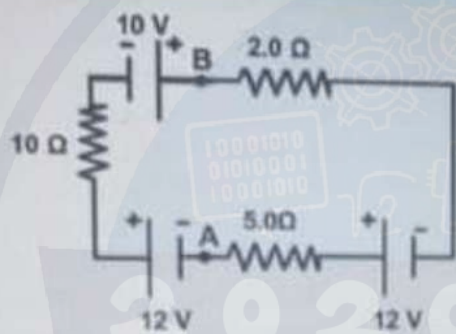



For the circuit shown, the potential of point A is 10 V. The potential of point B (in V) is:



Select one:

- 12
- 20
- 22
- 14
- 2

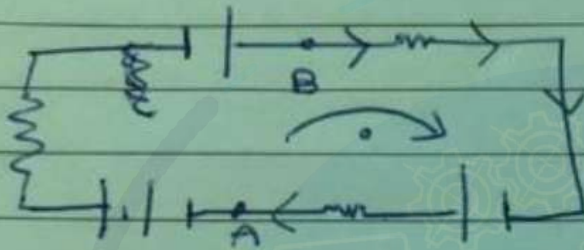② Given potential at point A $\Sigma V_A = 10V$



using KVL

$$10 - 2I + 12 - 5I + 12 - 10I = 0$$

$$34 - 17I = 0$$

$$I = \frac{34}{17} = 2A$$

$$-10 + 10(I) - 12 + (V_B - V_A) = 0$$

$$V_B - V_A = 22 - 10I$$


$$= 22 - 10(2)$$

$$V_B - V_A = 2$$

$$V_B = 2 + V_A = \boxed{12V}$$


The answer
is A

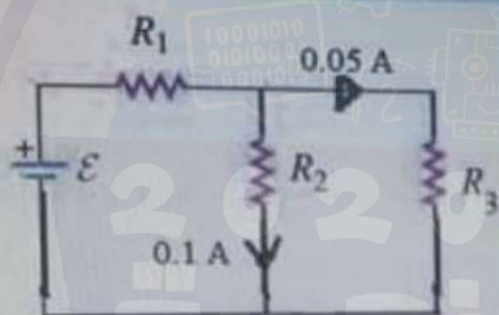For the circuit shown, $R_1 = 1.00 \text{ k}\Omega$, the emf of the battery is 5.0 V and its internal resistance is 1.00Ω . The power (in W) supplied by the battery is



Select one:

- 0.20
- 0.60
- 0.75
- 0.25
- 0.50

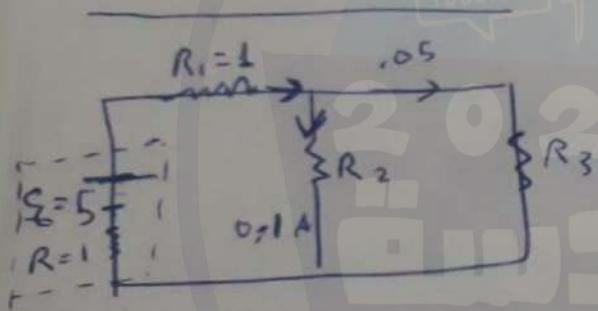


$$I_1 = I_2 + I_3 = 0.1 + 0.05 = 0.15 \text{ A}$$

$$P = IV = 0.15 \times 5 = 0.75 \text{ W}$$



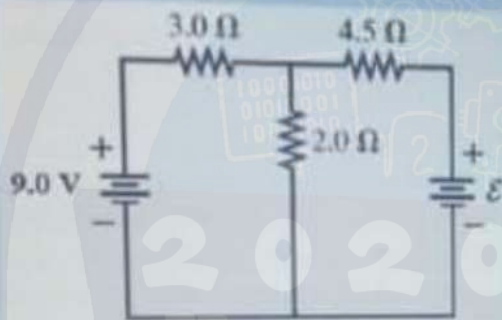
For the circuit shown, the current passing through the $4.5\ \Omega$ resistor is $2.0\ \text{A}$. Determine the power (in W) supplied by the unknown emf, \mathcal{E} .



Select one:

- 18
- 10
- 30
- 6
- 20

$$\xi = 5 + 2 = 10$$

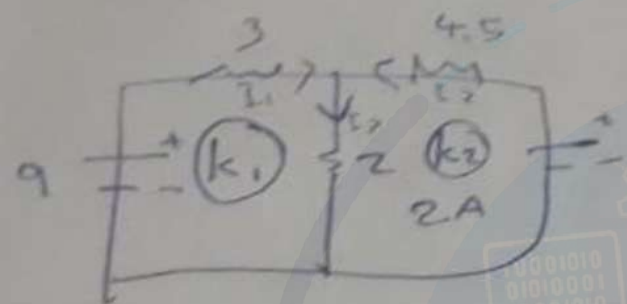

$$I_1 + I_2 = I_3$$

$$\Rightarrow I_2 = I_3 - I_1$$

$$I_3 - I_1 = 2$$

k: kerangka loop

$$k_1: 3I_1 - 9 + 2I_3 = 0 \quad \text{--- (1)}$$


$$k_2: 4.5 + 2 - \xi + 2I_3 = 0 \quad \text{--- (2)}$$

$$I_3 - I_1 = 2 \quad \text{--- (3)}$$

$$\rightarrow I_1 = 1A, \quad I_3 = 3A / \xi = 15V$$


$$P = VI = 15 \times 2 = 30W$$

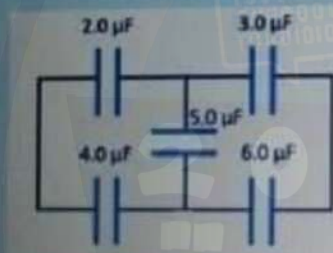In the circuit shown, if the charge stored by the $2.0 \mu\text{F}$ capacitor is $40 \mu\text{C}$, find the voltage across the $5.0 \mu\text{F}$ capacitor.



Select one:

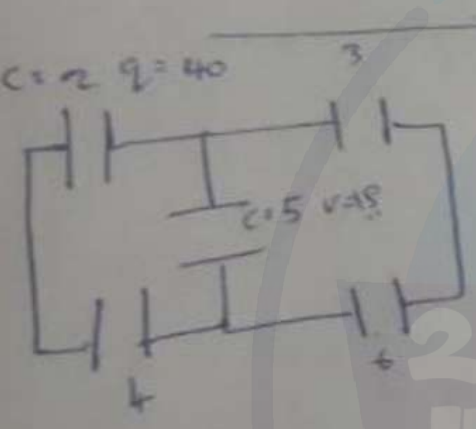- a. 15 V .
- b. 18 V .
- c. 9 V .
- d. 30 V .
- e. 0 V .



$C_1 \& C_4$ [series] so $Q_2 = Q_4$

$Q = CV$
 $\rightarrow V = \frac{Q}{C}$

$V_2 = \frac{40}{2} = 20$

$V_4 = \frac{40}{4} = 10$

$V_5 = V_2 + V_4 = 20 + 10 = 30V$

2020
 اساتذہ
 عزیزانہندسہ


A triangle is placed in a uniform magnetic field $B = 0.25 \text{ T}$ (the green arrow displayed in the figure). The current passing through the triangle (the blue arrow displayed in the figure) is 0.125 A . The magnetic force on the side AC has a magnitude of (in 10^{-2} N).




Select one:

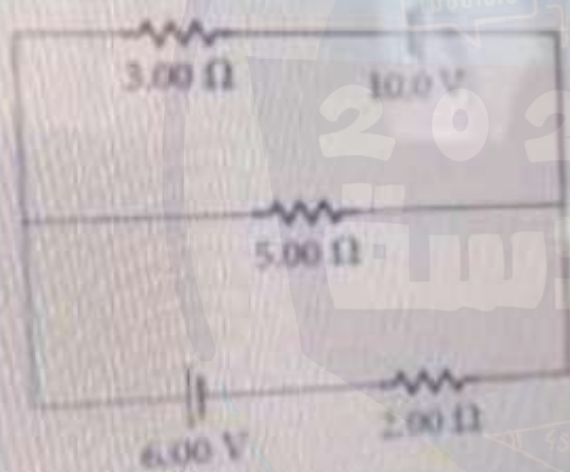- 4.22
- 1.17
- 2.22
- 1.47
- 3.52


For the circuit shown, determine the power (in W) delivered to the $5.00\ \Omega$ resistor



اسألني
2020
عن الامتحان

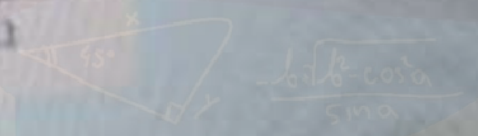

(k1) Kershoph loop

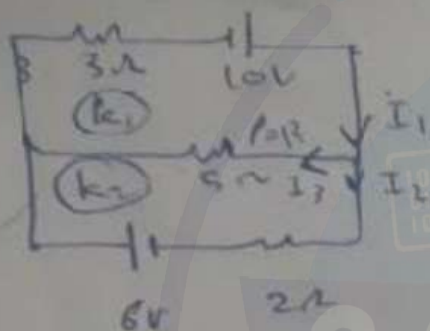

$$I_1 = I_2 + I_3$$

$$k_1: -10 + 3I_1 + 5I_2 = 0 \Rightarrow I_1 = \frac{10}{8}$$

$$k_2: 5I_3 - 2I_2 + 6 = 0$$


$$\rightarrow I_1 = 3.226 \text{ A}$$

$$I_2 = 3.161 \text{ A}$$

$$I_3 = -0.645 \text{ A}$$

$$P = I^2 R = (-0.645)^2 \cdot 5 = 0.208 \text{ W}$$

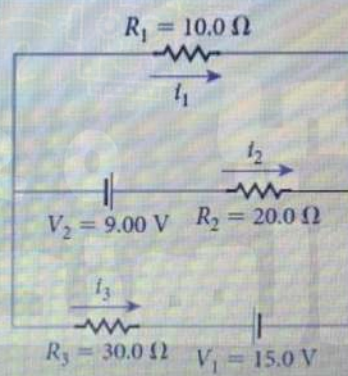
For the circuit shown, find the power (in W) dissipated in the resistor R_1 .



Select one:

0.0074

11.31

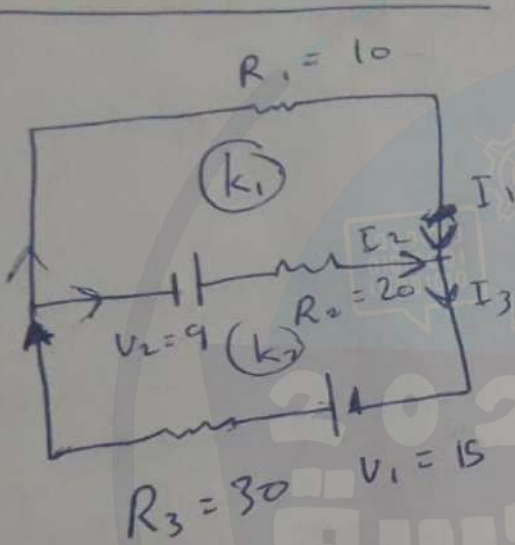

$$I_1 + I_2 = I_3$$

$$k_1: 10I_1 + 4 - 20I_2 = 0$$

$$k_2: 20I_2 - 9 + 30I_3 - 15 = 0$$

$$I_1 = .027 \text{ A}$$

$$I_2 = -.4636 \text{ A}$$

$$I_3 = .491 \text{ A}$$

$$P_{(R_1)} = R I^2 = 10 (.027)^2$$

$$= 7.29 \cdot 10^{-3} \text{ W}$$

A 102 PHY student has connected $[n]$ identical capacitors in parallel across a power supply of voltage 150.0 V. How many capacitors $[n]$, each with $C = 80.0 \mu\text{F}$, were connected to supply 114.3 J of energy? Report your result for $[n]$ as an integer number of capacitors.

Select one:

- 2023
- 402
- 489
- 127
- 13

[Clear my choice](#)

in parallel $\rightarrow \Rightarrow$ Vis equal an $C_{\text{equivalent}} = C_1 + C_2 + \dots$

$$C_{\text{eq}} = nC$$

$$\Rightarrow E = \frac{1}{2} C V^2 \Rightarrow 114.3 = \frac{1}{2} C_{\text{eq}} (150)^2$$

$$C_{\text{eq}} = 0.01016 \text{ F}$$

$$\rightarrow 0.01016 \text{ F} = n \cdot 80 \mu\text{F}$$

$$n = \frac{0.01016}{80 \cdot 10^{-6}} = 127$$

Which of the following is an **incorrect** statement?

Select one:

- The capacitance depends only on the geometry of the device and can never be negative quantity.
- The temperature coefficient of electric resistivity is a pure number with no dimension.
- The electromotive force has the same unit as the electric potential.
- The potential drops across electronic devices connected in parallel are equal.
- Ohm's law states that the ratio of the current density to the applied electric field is constant.

[Clear my choice](#)

The answer is A

A parallel plate capacitor consists of square plates of area 6.0 cm^2 separated by a distance of 2.0 mm . The capacitor is connected to a 6.0 V battery. If the plates are pulled apart so that the separation becomes 3.0 mm , how much work (in MeV) is done?


Select one:

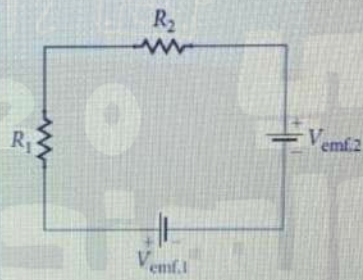- 18.61
- 5.05
- 808.03
- 789.47
- 99.56

[Clear my choice](#)




For the circuit shown, $R_1 = 23.37 \, \Omega$, $R_2 = 11.61 \, \Omega$, $V_{\text{emf},1} = 21.01 \, \text{V}$, and $V_{\text{emf},2} = 10.75 \, \text{V}$. Determine the current (in A) flowing through R_1 .



Select one:

0.293

0.007

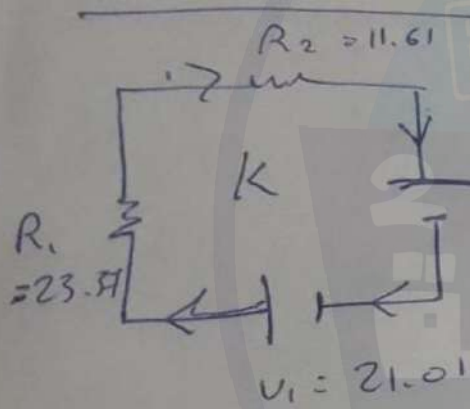

$$K \Rightarrow 11.61 I_1 + 23.37 I_1 - 21.01 + 10.75 = 0$$

$$\Rightarrow I_1 = -29.33 \text{ A}$$



A gold wire has a resistance R . If its length and diameter are both cut in half, its resistivity will:

Select one:

- decrease by a factor of 4
- increase by a factor of 4
- stay the same
- increase by a factor of 2
- decrease by a factor of 2

[Clear my choice](#)

The answer is C



A nickel wire has a resistance R . If its length and diameter are both reduced by a factor of 4, its resistivity will:

Select one:

- decrease by a factor of 4
- stay the same
- decrease by a factor of 16
- increase by a factor of 4
- increase by a factor of 16

The answer is B

A block of iron of volume 807 mm^3 is used to make a wire 23.7 m long. What is the resistance (in Ω) of such a wire at room temperature?

Take $\rho = 9.70 \times 10^{-8} \Omega \cdot \text{m}$

Select one:

- 0.07
- 67.51
- 504.78
- 1989.18
- 19.89

[Clear my choice](#)

$$R = \frac{PL}{A}$$

$$V = AL \Rightarrow A = \frac{V}{L}$$

$$R = \frac{PL}{\frac{V}{L}} \Rightarrow \frac{PL^2}{V} = \frac{9.7 \times 10^{-8} \times 23.7}{.807} = 67.51$$

Capacitors A and B are identical. Capacitor A is charged so it stores 4 J of energy and capacitor B is uncharged. The capacitors are then connected in parallel. The total stored energy (in J) in the capacitors is now:

*



(2 Points)

$\frac{1}{4}$


16

8

4

2

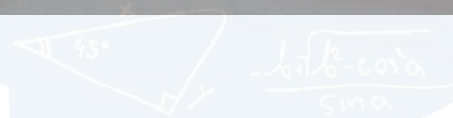Parallel so $V_1 = V_2$ and $C_1 = C_2$
then $C_1 = C_2$ and the voltage will drop by 2
 $\Rightarrow V_s = 2V$



A parallel plate capacitor consists of square plates of area 3.0 cm^2 separated by a distance of 3.0 mm . The capacitor is connected to a 6.0 V battery. If the plates are brought closer so that the separation becomes 2.0 mm , how much work (in MeV) is done?

Select one:

- 408.37
- 1111.78
- 49.78
- 423.09
- 2.88

اسألني
2020
عن الهندسة

A 102 PHY student has connected $[n]$ identical capacitors in parallel across a power supply of voltage 210.0 V. How many capacitors $[n]$, each with $C = 45.0 \mu\text{F}$, were connected to supply 231.2 J of energy? Report your result for $[n]$ as an integer number of capacitors.

Select one:

- 404
- 465
- 27
- 233
- 911

$$C_{eq} = \frac{1}{2} n C$$

$$E = \frac{1}{2} C U^2$$

$$231.2 = \frac{1}{2} n \cdot 45 \cdot 10^{-6} \cdot 210^2$$

$$n = \underline{\underline{233}}$$

Useful Constants

$k_e = 1/4\pi\epsilon_0 = 9 \times 10^9 \text{ N}\cdot\text{m}^2/\text{C}^2$; $\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2/\text{N}\cdot\text{m}^2$; $e = 1.6 \times 10^{-19} \text{ C}$; $m_{\text{electron}} = 9.11 \times 10^{-31} \text{ kg}$; $m_{\text{proton}} = 1.67 \times 10^{-27} \text{ kg}$; $g = 9.8 \text{ m/s}^2$


If a potential difference of 2 V is applied across a 1- μF capacitor, then the charge (in μC) on the capacitor is

- a. 2
- b. 4
- c. 6
- d. 8
- e. 10

Useful Constants

$k_e = 1/4\pi\epsilon_0 = 9 \times 10^9 \text{ N}\cdot\text{m}^2/\text{C}^2$; $\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2/\text{N}\cdot\text{m}^2$; $e = 1.6 \times 10^{-19} \text{ C}$; $m_{\text{electron}} = 9.11 \times 10^{-31} \text{ kg}$; $m_{\text{proton}} = 1.67 \times 10^{-27} \text{ kg}$; $g = 9.8 \text{ m/s}^2$

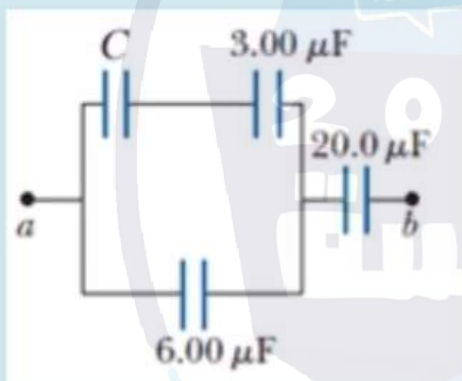
Four capacitors are connected as shown in the figure. If $C = 3.0 \mu\text{F}$, the equivalent capacitance (in μF) between points a and b is



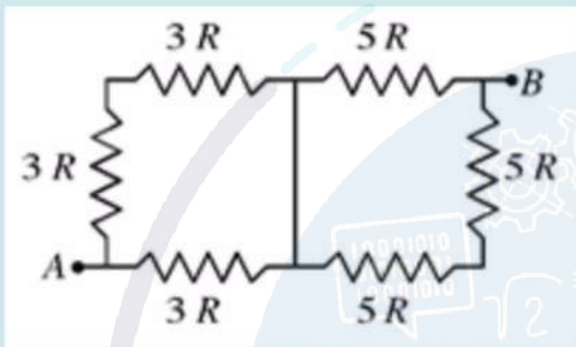- a. 6.0
- b. 5.7
- c. 5.5
- d. 5.0
- e. 5.3


10^{-27} kg; $g = 9.8$ m/s²

If $R = 9 \Omega$, what is the equivalent resistance (in Ω) between points A and B in the figure?



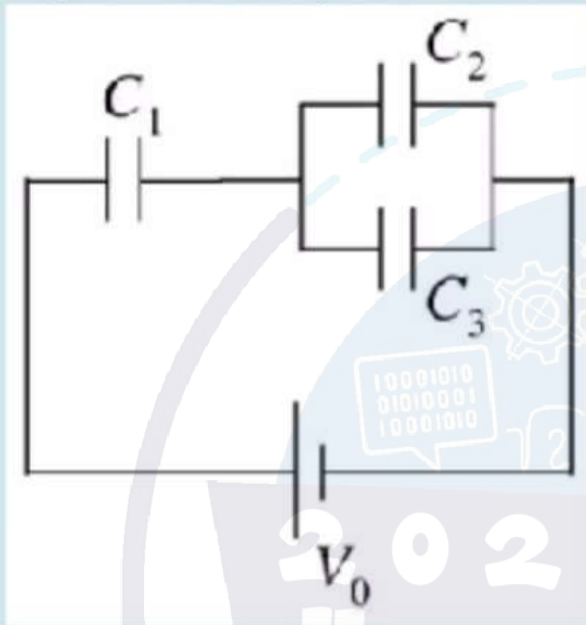- a. 64
- b. 96
- c. 112
- d. 48
- e. 32

Determine the charge stored by C_1 (in mC) when $C_1 = 20 \mu\text{F}$, $C_2 = 10 \mu\text{F}$, $C_3 = 30 \mu\text{F}$, and $V_0 = 36 \text{ V}$.




- a. 0.36
- b. 0.24
- c. 0.32
- d. 0.4
- e. 0.48

10^{-27} kg; $g = 9.8$ m/s²

A potential difference of 7.0 V is applied across a cylindrical conductor. The conductor is 20.0 m long, and has a radius of 0.5 mm and a resistivity of 5.6×10^{-8} $\Omega \cdot \text{m}$. The current flowing in the conductor (in A) is

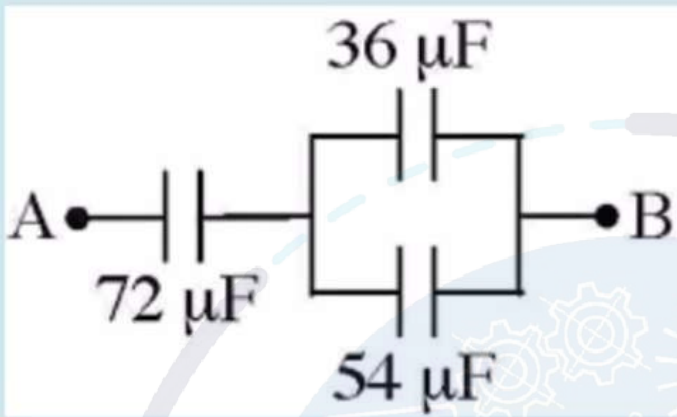
- a. 1.4
- b. 2.5
- c. 4.2
- d. 4.9
- e. 6.1

If $V_A - V_B = 60 \text{ V}$, how much energy (in mJ) is stored in the $54\text{-}\mu\text{F}$ capacitor?



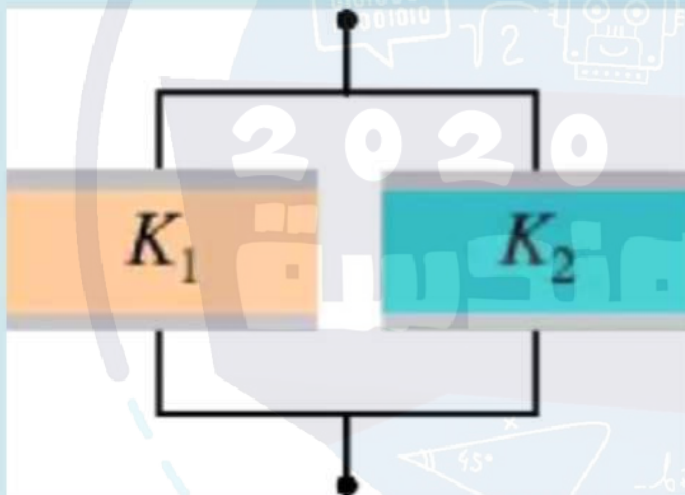- a. 50.3
- b. 13.3
- c. 26.1
- d. 34.1
- e. 19.2

Two identical parallel-plate capacitors each having plate area $A = 50.0 \text{ cm}^2$ and plate separation $d = 1.0 \text{ mm}$ are completely filled with two different dielectrics of dielectric constants $K_1 = 2.0$ and $K_2 = 5.5$, and then connected as shown in the figure. The equivalent capacitance (in pF) of the combination is




- a. 221
- b. 266
- c. 332
- d. 389
- e. 416

A capacitor in a single-loop RC circuit is charged to 85% of its final potential difference in 3.2 s. What is the time constant (in s) for this circuit?

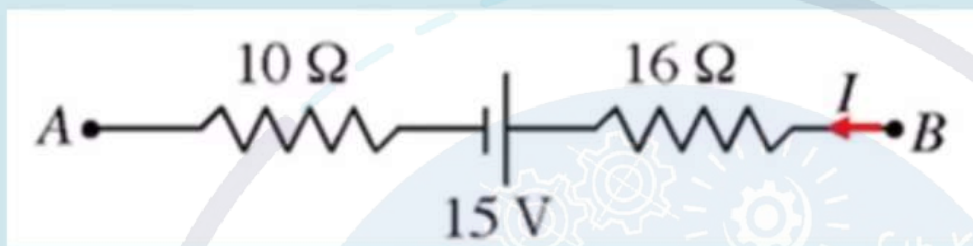
- a. 1.27
- b. 0.79
- c. 2.11
- d. 1.69
- e. 2.64

What is the potential difference $V_B - V_A$ (in V) when $I = 2.0$ A in the circuit segment shown below?



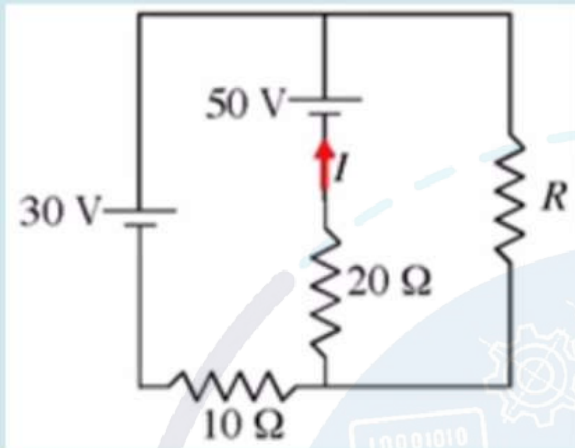- a. +54
- b. +67
- c. -54
- d. -67
- e. +18

Determine the resistance R (in Ω) when $I = 2.0$ A.




- a. 8
- b. 30
- c. 2.5
- d. 4.1
- e. 16.3

Useful Constants

$k_e = 1/4\pi\epsilon_0 = 9 \times 10^9 \text{ N}\cdot\text{m}^2/\text{C}^2$; $\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2/\text{N}\cdot\text{m}^2$; $e = 1.6 \times 10^{-19} \text{ C}$; $m_{\text{electron}} = 9.11 \times 10^{-31} \text{ kg}$; $m_{\text{proton}} = 1.67 \times 10^{-27} \text{ kg}$; $g = 9.8 \text{ m/s}^2$

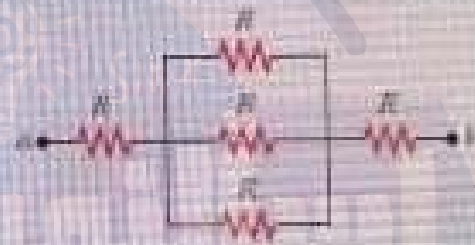What is the equivalent resistance (in Ω) of the combination of identical resistors between points a and b in the figure if $R = 18 \Omega$.



35

a

28 b

42

c

49

d

56 e

Useful Constants

$k_e = 1/4\pi\epsilon_0 = 9 \times 10^9 \text{ N}\cdot\text{m}^2/\text{C}^2$; $\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2/\text{N}\cdot\text{m}^2$; $e = 1.6 \times 10^{-19} \text{ C}$; $m_{\text{electron}} = 9.11 \times 10^{-31} \text{ kg}$; $m_{\text{proton}} = 1.67 \times 10^{-27} \text{ kg}$; $g = 9.8 \text{ m/s}^2$

If a potential difference of 40 V is applied across a 10- Ω resistor, then the current (in A) flowing in the resistor is

4.0

2.0

4.0


4.0

5.0

Useful Constants

$k_e = 1/4\pi\epsilon_0 = 9 \times 10^9 \text{ N}\cdot\text{m}^2/\text{C}^2$; $\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2/\text{N}\cdot\text{m}^2$; $e = 1.6 \times 10^{-19} \text{ C}$; $m_{\text{electron}} = 9.11 \times 10^{-31} \text{ kg}$; $m_{\text{proton}} = 1.67 \times 10^{-27} \text{ kg}$; $g = 9.8 \text{ m/s}^2$

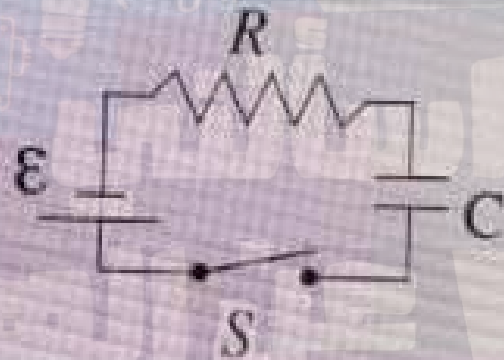The capacitor in the figure is initially uncharged. If $R = 15.0 \text{ k}\Omega$, $\mathcal{E} = 24.0 \text{ V}$, and the time constant is $\tau = 55.0 \mu\text{s}$, then after closing the switch the time (in μs) it takes for the voltage across the capacitor to reach 8.0 V is



10

a

22

38 b


60

c

d

99 e

3

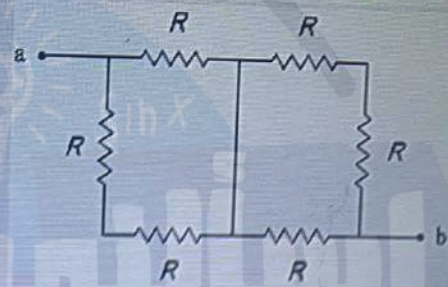

In the figure, if $R = 12 \Omega$, the equivalent resistance (in Ω) between points a and b is: *
(2 Points)

- 16
- 6
- 24
- 28
- 20


8

A parallel plate capacitor with a capacitance of $12 \mu\text{F}$ is connected to a source of emf with a potential difference of 3 V . If a dielectric material of $\kappa = 6$ is inserted between the plates of the capacitor, then the change in the stored electrical energy, ΔU (in J) is: *

(2 Points)

- 0
- 1.2×10^{-5}
- 1.4×10^{-6}
- 5.4×10^{-5}
- 2.7×10^{-5}

اساسي 2020
عن الهندسة

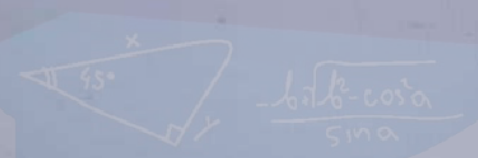


2


A $10.0 \mu\text{F}$ capacitor is charged using a 10.0 V battery through a resistor R . If the potential difference on the capacitor reaches 4.00 V in 3.00 sec , then R (in $\text{k}\Omega$) is : *

(2 Points)

- 1.35
- 391
- 587
- 402
- 108

اسألني
2020
عن الهندسة

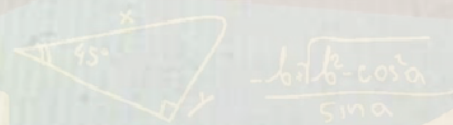


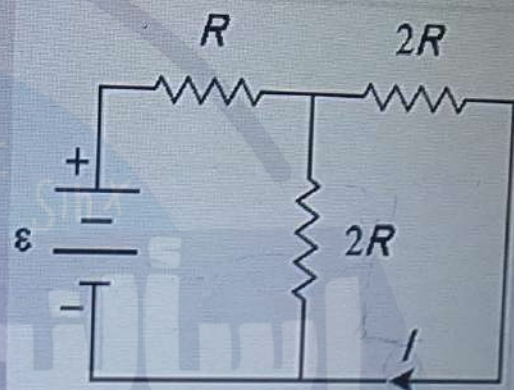

In the figure shown, if $I = 0.50 \text{ A}$ and $R = 12 \Omega$, determine ϵ (in Volt). * (2 Points)


- 24
- 12
- 6
- 30

5

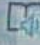A $10.0 \mu\text{F}$ capacitor is charged using a 10.0 V battery through a resistor R . If the potential difference on the capacitor reaches 4.00 V in 3.00 sec , then R (in $\text{k}\Omega$) is : * 
(2 Points)

- 402
- 108
- 587
- 1.35
- 391

5

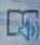A $10.0 \mu\text{F}$ capacitor is charged using a 10.0 V battery through a resistor R . If the potential difference on the capacitor reaches 4.00 V in 3.00 sec , then R (in $\text{k}\Omega$) is : * 
(2 Points)

402



108


587

1.35

391

6

2

A parallel plate capacitor with a capacitance of $12 \mu\text{F}$ is connected to a source of emf with a potential difference of 3 V . If a dielectric material of $\kappa = 6$ is inserted between the plates of the capacitor, then the change in the stored electrical energy, ΔU (in J) is: * 
(2 Points)


- 1.4×10^{-6}
- 1.2×10^{-5}
- 2.7×10^{-4}
- 5.4×10^{-5}
- 0

4

Two spheres are made of conducting material. Sphere #2 has twice the radius of sphere #1. What is the ratio of the capacitance of sphere #2 to the capacitance of sphere #1? *
(2 Points)

- $\frac{1}{4}$
- 1
- 4
- 2
- None of the above is correct

9

A $12.0 \mu\text{F}$ capacitor is charged to a potential of 50.0 V and then discharged through a $225\text{-}\Omega$ resistor. How long does it take the capacitor to lose half of its stored energy? * 
(2 Points)

- 1.871 ms
- 0.936 ms
- None of the above*
- 0.468 ms
- 0.234 ms


required


1

A long copper wire of cross sectional area of $4.0 \times 10^{-6} \text{ m}^2$ and carrying a current of 5 A. The drift speed in (m/s) of the electrons in wire is : (the concentration of electrons is $6.0 \times 10^{28} / \text{m}^3$, $e = 1.6 \times 10^{-19} \text{ C}$) *
(2 Points)

- 4.0×10^{-4}
- 0.13×10^{-4}
- None of the above
- 13×10^{-4}
- 1.3×10^{-4}

اسألني
2020
عن الهندسة

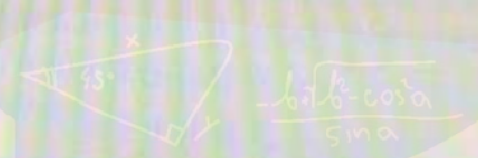

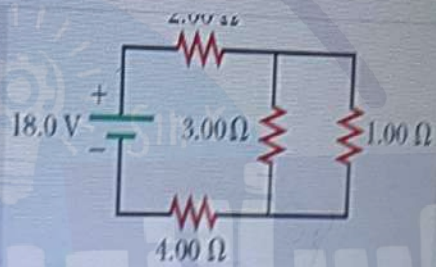

What is the current (in A) in the 1.00-Ω resistor shown in the figure? *
(2 Points)

- 3.00
- 0.67
- 2.42
- 2.00
- 0.30

Activate Windows
Go to Settings to activate Windows.

9

A $12.0 \mu\text{F}$ capacitor is charged to a potential of 50.0 V and then discharged through a $225\text{-}\Omega$ resistor. How long does it take the capacitor to lose half of its stored energy? * (2 Points)

- 1.871 ms
- 0.936 ms
- None of the above*
- 0.468 ms
- 0.234 ms

13

$$\Delta V = 2 \text{ V} \quad C = 1 \text{ mF} \quad q = ???$$

$$C = \frac{q}{\Delta V} \Rightarrow q = 2 * 1 * 10^{-6}$$



$$q = \boxed{2 \text{ mC}} \quad \text{a}$$

Q₂

$$C = 3 \text{ } \mu\text{f}$$


(C, 3) (series)
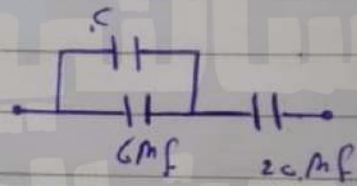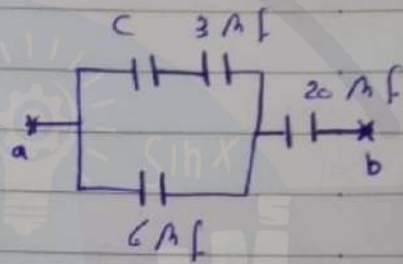
$$C_1 = \frac{3 \times 10^{-6} \times 3 \times 10^{-6}}{6 \times 10^{-6}} = \frac{3}{2} \times 10^{-6} \text{ f}$$




(C₁, 6) (parallel)
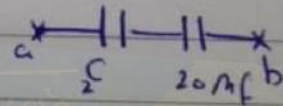
$$C_2 = \frac{3}{2} \times 10^{-6} + 6 \times 10^{-6} = 7.5 \times 10^{-6} \text{ f}$$



(C₂, 20) (series)

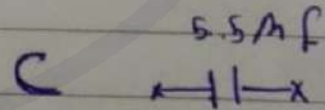
$$C_q = \frac{7.5 \times 10^{-6} \times 20 \times 10^{-6}}{27.5 \times 10^{-6}} = \boxed{5.5 \times 10^{-6} \text{ f}}$$



(1, 2) (5, 4) (series)

① $5R + 5R = 10R = R_1$


② $3R + 3R = 6R = R_2$

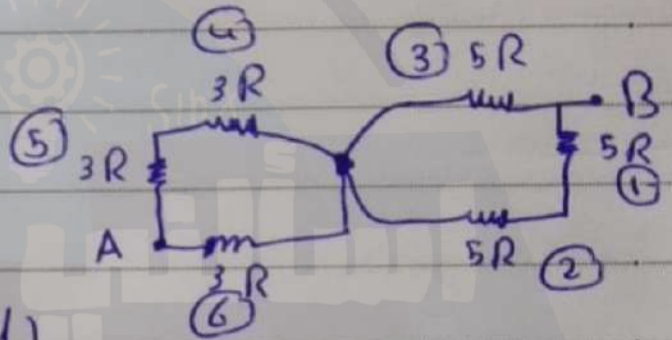

(R₁, 5R) (R₂, 3R) (Parallel)

① $\frac{10R * 5R}{10R + 5R} = \frac{50R^2}{15R} = 3.33R = R_3$

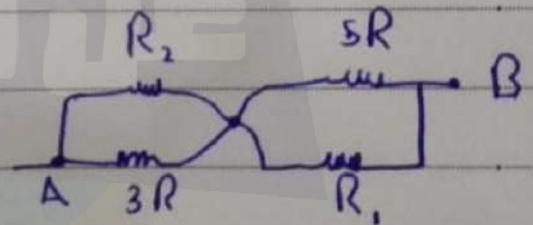
② $\frac{6R * 3R}{6R + 3R} = \frac{18R^2}{9R} = 2R = R_4$



(R₃, R₄) (series)

$3.33R + 2R = 5.33R \Rightarrow 5.33 * 9 = 48$


(d)

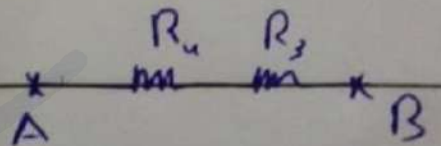

$$C_1 = 20 \mu\text{f} \quad C_2 = 10 \mu\text{f} \quad C_3 = 30 \mu\text{f}$$


$$V_0 = 36 \text{V}$$

(C_2, C_3) (Parallel)

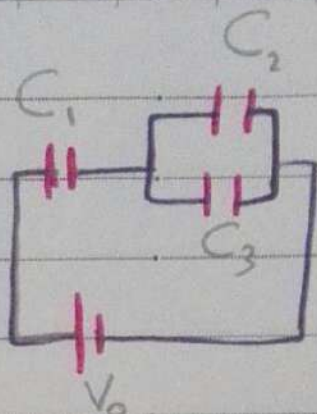


$$(10 + 30) \times 10^{-6} = 40 \times 10^{-6} \text{f} = C_4$$

(C_1, C_4) (series)

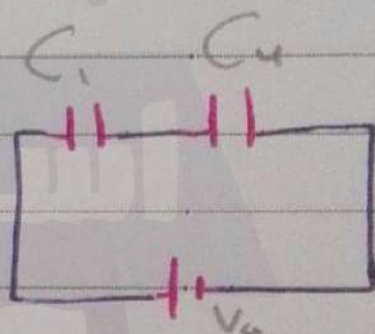

$$\frac{40 \times 10^{-6} \times 20 \times 10^{-6}}{(40 + 20) \times 10^{-6}} = \frac{800}{360} \times 10^{-6}$$

$$= \frac{40}{3} \mu\text{f} = C_{eq}$$

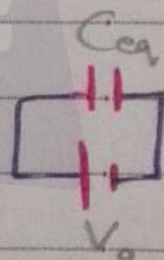


$$I_{tot} = C * V \Rightarrow \bar{I}_{tot} = \frac{40 \times 10^{-6}}{3} \times 36 =$$

$$\Rightarrow \bar{I}_{tot} = 480 \text{mA}$$

$$\bar{I}_{inc} = 48 \text{mC} \quad e$$

5

$$\rho = 5.6 \times 10^{-8}$$

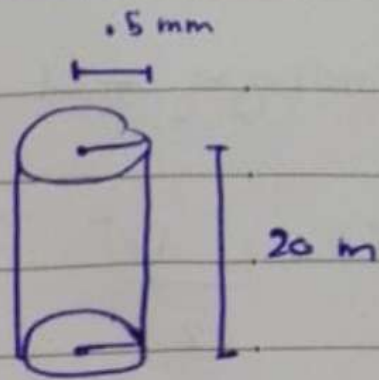

$$R = \frac{\rho L}{A}$$

$$R = \frac{5.6 \times 10^{-8} \times 20}{\pi \times (0.5 \times 10^{-3})^2}$$

$$R = 1.426$$

$$R = \frac{V}{I} \Rightarrow I = \frac{7}{1.426} = 4.9$$


$$I = 4.9$$

d)

6


(36, 54) (Parallel)
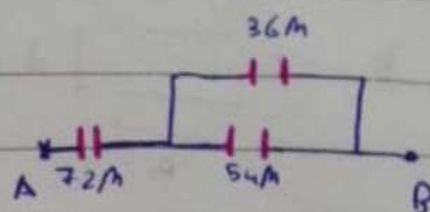
$$36 + 54 = \boxed{90 \text{ } \mu\text{F}} = C$$



(C, 72) (Series)

$$\frac{90 \times 10^{-6} \times 72 \times 10^{-6}}{(90 + 72) \times 10^{-6}} = \boxed{40 \times 10^{-6}} = C_a$$

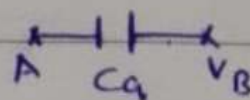~~V in C, 80~~

$$C = \frac{q}{\Delta V} \Rightarrow q = 40 \times 10^{-6} \times 60 \Rightarrow \boxed{q_{\text{tot}} = 24 \times 10^{-4}}$$

V in C, 80

$$V = \frac{24 \times 10^{-4}}{90 \times 10^{-6}} = \frac{4}{15} \times 100 = \boxed{\frac{80}{3} \text{ V}}$$

$$V \text{ in } (54 \mu\text{F}) = \frac{80}{3}$$


$$\text{energy} = \frac{CV^2}{2} \Rightarrow U = \frac{54 \times 10^{-6} \times \left(\frac{80}{3}\right)^2}{2}$$

$$\boxed{U = 19.2 \text{ mJ}}$$

التوصيل على التوازي :-

$$\epsilon_0 = 8.85 \times 10^{-12}$$
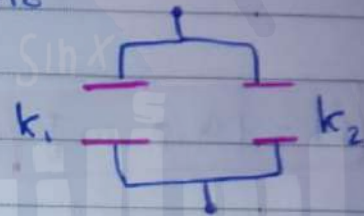
$$C_{eq} = \frac{k_1 \times A \times \epsilon_0}{d} + \frac{k_2 \times A \times \epsilon_0}{d}$$



$$C_{eq} = (k_1 + k_2) \frac{A \times \epsilon_0}{d}$$

$$k_1 = 2 \quad A = 50 \text{ cm}^2 \quad d = 1 \text{ mm}$$

$$k_2 = 5.5 \quad A = 50 \text{ cm}^2 \quad d = 1 \text{ mm}$$

$$= \frac{(2 + 5.5) \times 50 \times 10^{-4} \times 8.85 \times 10^{-12}}{1 \times 10^{-3}}$$

$$= \frac{7.5 \times 50 \times 10^{-4} \times 8.85 \times 10^{-12}}{1 \times 10^{-3}} = 331.875 \times 10^{-12} \approx \boxed{332 \text{ pF}}$$

$$v(t) = \mathcal{E} (1 - e^{-\frac{t}{\tau}})$$

$$.85 \mathcal{E} = \mathcal{E} (1 - e^{-\frac{t}{\tau}})$$

$$.85 - 1 = e^{-\frac{t}{\tau}}$$

$$+0.15 = + e^{-\frac{t}{\tau}}$$

$$\ln 0.15 = \ln e^{-\frac{t}{\tau}}$$

$$-1.9 = -\frac{3.2}{\tau}$$


$$\tau = \frac{3.2}{1.9} = 1.69 \text{ (d)}$$

Q2a

$$V_A + 10I + 15 + 16I = V_B$$

$$V_B - V_A = 67$$

(b)

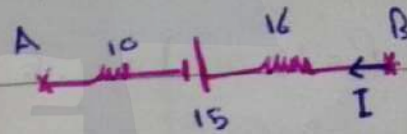

$$I = 2A$$

10

$$I = 2$$

$$10- V_a + 10I_1 + 30 - 50 + 20I = V_a$$

$$10I_1 - 20 + 40 = 0$$


$$I_1 = \frac{-20}{10} = \boxed{-2}$$

$$V_a - 20I + 50 - R(I - I_1) = V_a$$

$$-40 + 50 - R(4) = 0$$

$$4R = 10 \Rightarrow R = \frac{10}{4}$$

$$\boxed{R = 2.5}$$

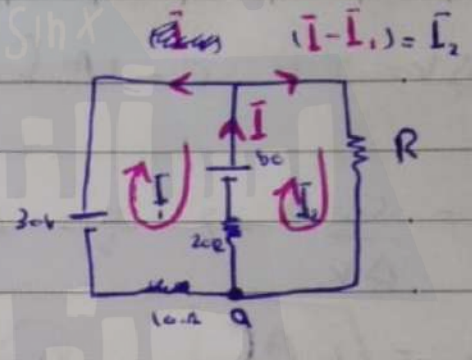

$$V_B - V_A = 67$$


(b)

$$I = 2A$$

(2, 3, 4) (Parallel)

$$\frac{1}{R} + \frac{1}{R} + \frac{1}{R} = \frac{1}{R_1}$$
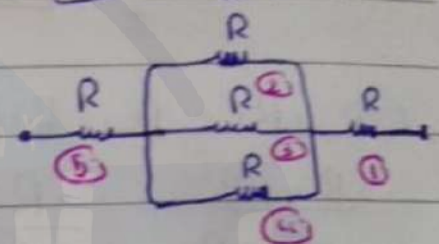
$$\frac{3}{R} = \frac{1}{R_1} \Rightarrow R_1 = \frac{R}{3}$$




(1, R₁, 5) (series)

$$R + R_1 + R \Rightarrow R + \frac{R}{3} + R =$$

$$= 2R + \frac{R}{3} = \frac{7R}{3}$$
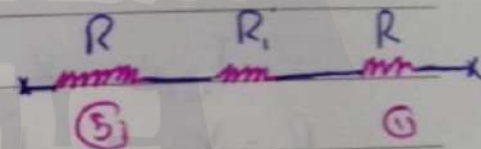
$$\Rightarrow \frac{7}{3} \times 18 = 42 \quad (c)$$



12

$V = 40\text{ V}$ $R = 10\ \Omega$ $\bar{I} = ???$

$$R = \frac{V}{I} \Rightarrow \bar{I} = \frac{40}{10} = 4\text{ A}$$

$$\bar{I} = 4\text{ A}$$

d

$$V = E \left(1 - e^{-\frac{t}{RC}} \right)$$

$$\Rightarrow 8 = 24 \left(1 - e^{-\frac{t}{RC}} \right)$$

$$\frac{1}{3} - 1 = -e^{-\frac{t}{RC}}$$

$$\frac{2}{3} = e^{-\frac{t}{RC}}$$


$$-0.4055 = \frac{-t}{55 \times 10^{-6}}$$

$$t = 22 \mu s$$

(1, 2) (4, 5) (series)

① $R + R = 2R = R_1$


② $R + R = 2R = R_2$

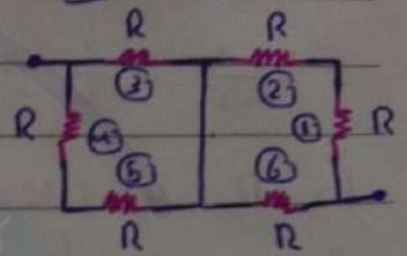

(R₁, 6) (3, R₂) (parallel)

① $\frac{2R * R}{2R + R} = \frac{2R^2}{3R} = \frac{2}{3}R = R_3$

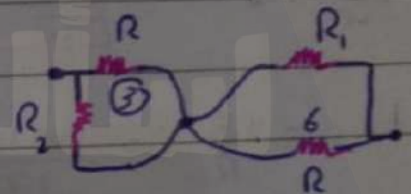② $\frac{2R * R}{2R + R} = \frac{2}{3}R = R_4$



(R₃, R₄) (series)

$\frac{2}{3}R + \frac{2}{3}R = \frac{4}{3}R \Rightarrow \frac{4}{3} * 12 = 16$

energy = U

$$U = \frac{C V^2}{2}$$

$$U_1 = \frac{12 \times 10^{-6} \times 9}{2} = 54 \times 10^{-6} \text{ J}$$

$$U_2 = \frac{C_{\text{new}} V^2}{2}$$

$$C_{\text{new}} = C k$$

$$C_{\text{new}} = 12 \times 10^{-6} \times 6 = 72 \times 10^{-6} \text{ f}$$

$$U_2 = \frac{72 \times 10^{-6} \times 9}{2} = 324 \times 10^{-6} \text{ J}$$

$$\Delta U = U_2 - U_1$$

$$\Delta U = 324 \times 10^{-6} - 54 \times 10^{-6} = 270 \times 10^{-6} \text{ J}$$

$$\Delta U = 2.7 \times 10^{-4} \text{ J}$$

$$V = 4 \text{ V} \quad \mathcal{E} = 10 \text{ V} \quad C = 10 \text{ mF} \quad t = 3 \text{ s}$$

$$V(t) = \mathcal{E} \left(1 - e^{-\frac{t}{RC}} \right)$$

$$4 = 10 \left(1 - e^{-\frac{3}{R \times 10 \times 10^{-6}}} \right)$$

$$\frac{4}{10} = 1 - e^{-\frac{3}{R \times 10 \times 10^{-6}}}$$

$$\ln(1 - 0.6) = \ln \left(e^{-\frac{3}{R \times 10 \times 10^{-6}}} \right)$$

$$-0.510826 = \frac{-3}{R \times 10 \times 10^{-6}}$$

$$\boxed{R = 587 \Omega}$$

$$R = 12 \quad I = .5$$

-> ① \bar{I} في المقاومة

$$2R = \frac{V}{I} \Rightarrow V = 2R \times \bar{I}$$

$$V = 2 \times 12 \times \frac{1}{2} = \boxed{12V}$$

(2R, 2R) (Parallel)

$$\frac{2R \times 2R}{2R + 2R} = \frac{4R^2}{4R} = \boxed{R} = R_1$$



-> \bar{I}_{tot} في R_1 هو 2

$$R_1 = \frac{V}{\bar{I}_{tot}} \Rightarrow \bar{I}_{tot} = \frac{12}{R} = \frac{12}{12} = \boxed{1A}$$

(R, R) (series)

$$R + R = 2R$$
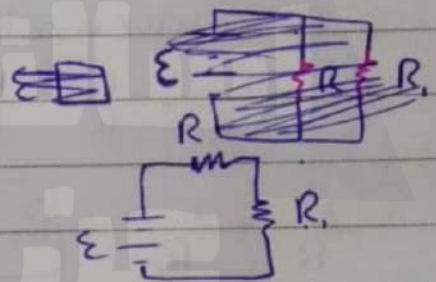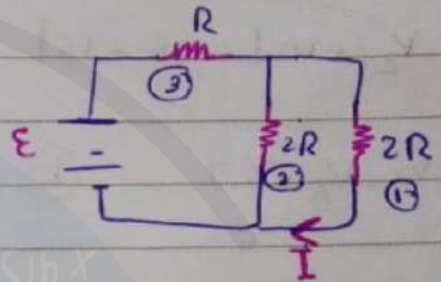
$$\varepsilon = 2R \times \bar{I}_{tot} = 2R = \boxed{24}$$



$$\text{energy} = U$$

المعادلة الأولى

$$U_{\text{old}} = \frac{Q^2}{2C}$$

$$Q = CV = 12 \times 10^{-6} \times 50$$

$$Q_{\text{max}} = 600 \times 10^{-6} \text{ C}$$

$$U = \frac{(600 \times 10^{-6})^2}{2 \times 12 \times 10^{-6}} = \boxed{15 \times 10^{-3} \text{ J}}$$

المعادلة الثانية

$$U_{\text{new}} = 7.5 \times 10^{-3}$$

$$U = \frac{Q^2}{2C}$$
$$\Rightarrow \frac{7.5 \times 10^{-3}}{1} = \frac{Q^2}{2 \times 12 \times 10^{-6}}$$

$$Q = \sqrt{180 \times 10^{-9}} \Rightarrow Q = 424.2641 \times 10^{-6}$$

$$Q(t) = Q_{\text{max}} e^{-\frac{t}{RC}}$$

$$424.2641 \times 10^{-6} = 600 \times 10^{-6} \times e^{-\frac{t}{RC}}$$

$$\ln 0.70711 = \ln e^{-\frac{t}{RC}}$$

$$+0.34657 = -\frac{t}{RC}$$

$$225 \times 12 \times 10^{-6}$$

$$t = 935.75 \times 10^{-6}$$

$$\boxed{t = 0.936 \text{ ms}}$$

$$A = 4 \times 10^{-6} \text{ m}^2 \quad \bar{I} = 5 \text{ A} \quad q = 1.6 \times 10^{-19} \text{ C} \quad N = 6 \times 10^{28}$$

$$\bar{I} = N \cdot |q| \cdot V_d \cdot A$$


$$5 = 6 \times 10^{28} \cdot 1.6 \times 10^{-19} \cdot V_d \cdot 4 \times 10^{-6}$$

$$5 = 38.4 \times 10^3 V_d$$

$$V_d = 1.3 \times 10^{-4}$$


(1, 3) Ω (Parallel)
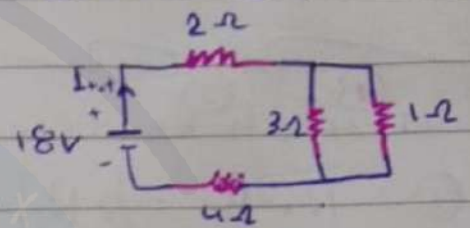
$$\frac{1 \times 3}{1+3} = \frac{3}{4} \Omega = R_1$$



(2, R₁, 4) (series)
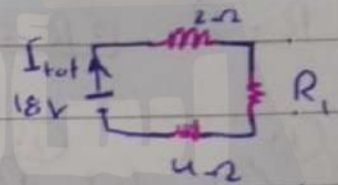
$$\frac{3}{4} + 2 + 4 = \frac{27}{4} = R_Q$$



$$I_{tot} = \frac{18}{R_Q} = \frac{4 \times 18^2}{27} = \frac{8}{3} \text{ A}$$

$$V \text{ in } R_1 \Rightarrow V = I_{tot} * R_1 = \frac{8}{3} * \frac{3}{4} = 2 \text{ V} = V \text{ in } (1-2)$$

$$I \text{ in } (1-2) \Rightarrow I = \frac{2}{1} = 2 \text{ A}$$