

LAB REPORT FOR EXPERIMENT 4

10

Date: -----

Name: -----

Partner's Name

Registration No: ---

Registration No: ---

Physics Section: ---

Instructor's Name: ---

PHYSICS LAB EXPERIMENT 4: POWER TRANSFER

I. PURPOSE

to find the condition under which maximum power is transferred to the load resistance that connected across a power source.

II. DATA AND DATA ANALYSIS:

1. Use the equation $P = VI$ to calculate P_L the power dissipated by the load resistor R_L and enter the calculated values in Table (4.1) below:

Table 4.1

$R_s = 100 \Omega$				
Reading	$R_L (\Omega)$	I_L (mA)	V_L (V)	P_L (mW)
1	20	54	0.8	43.2
2	40	46	1.5	69
3	60	40	2	80
4	80	36	2.2	79.2
5	100	31	2.8	86.8
6	200	21	3.7	77.7
7	400	12	4.4	52.8
8	600	10	4.7	47
9	800	8	4.9	39.2

2. Plot on a graph paper the power P_L as dependent variable versus the load resistor R_L . Find the value of the load resistor for which the power dissipated is **maximum**. How is this value related to the series resistance R_s .

$$R_L = 100 \quad \text{and} \quad \boxed{R_L = R_s}$$

3. For what value of the load resistance R_L was:

1) The load current a maximum? 20Ω

2) The load voltage a maximum? 300Ω

4. Using the expression for P_L power dissipated in the load resistance as a function of the load resistance R_L , determine the condition for the maximum power (differentiate P_L with respect to R_L and set $\frac{dP_L}{dR_L} = 0$)

$$P_L = I^2 R$$

$$I = \frac{V}{R}$$

$$\frac{dP}{dR_L} = \frac{U^2 R_L / (R_s + R_L)^2 - U^2 (R_L + R_s)^2}{(R_L + R_s)^4} = 0$$

$$(R_s + R_L)^2 / 2 = 2 R_L (R_s + R_L)$$

$$R_s + R_L = 2 R_L$$


$$\boxed{R_s = R_L}$$

- 5- Compare the value of R_L at maximum power found in (2) with that found in (4) above.

the same result

- 6- If the internal resistance, R_s , is larger than the load resistance R_L , which resistance will dissipate more power?

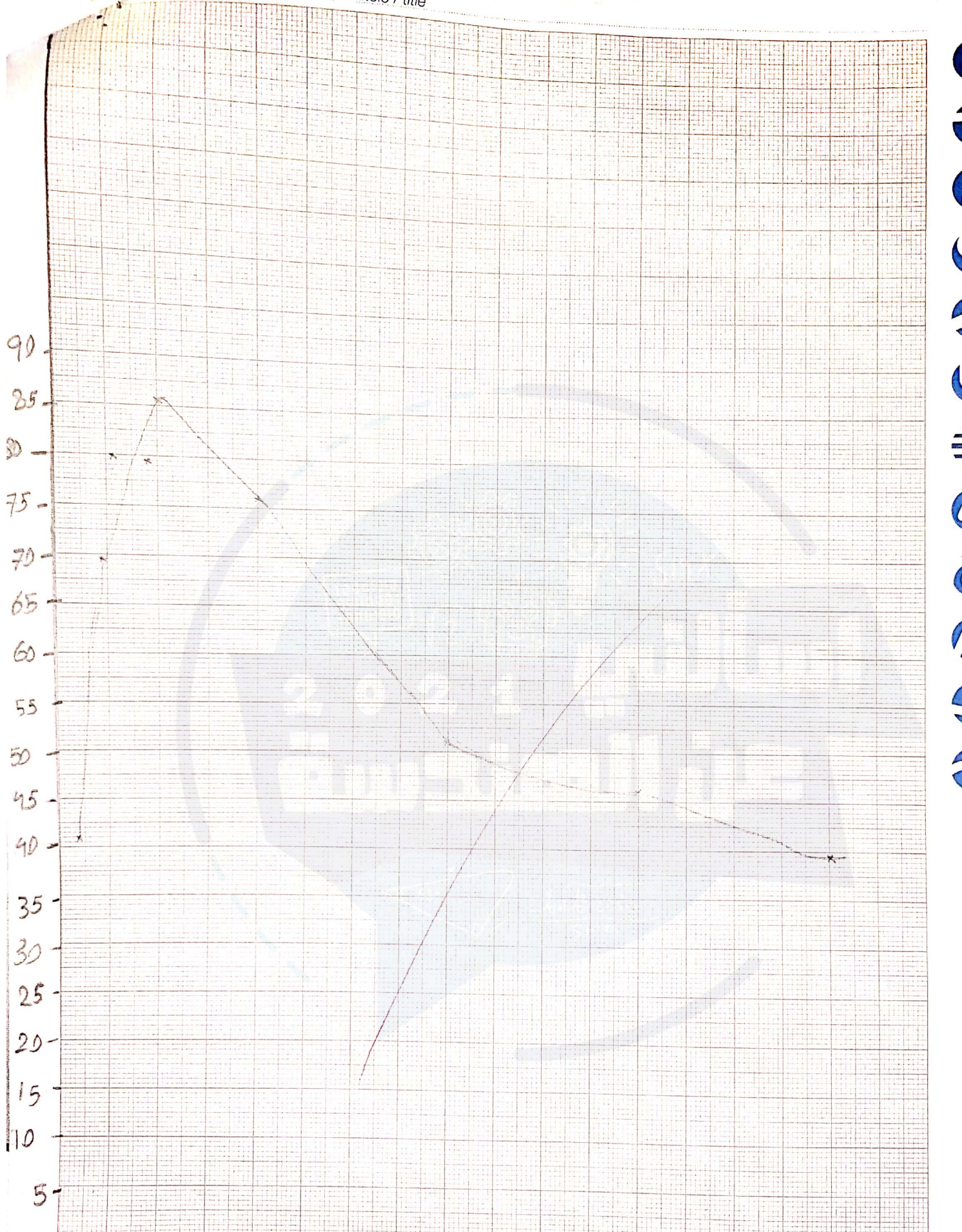$R_s > R_L$ $P_s = I^2 R_s$, $P_L = I^2 R_L$ (the same current)
 R_s will dissipate more power.




VALSIR S.p.A.
 Località Oleggio, 2
 25078 Vestone (BS) - Italy
 Tel. +39 0365 877.011
 Fax +39 0365 81.268
 P.IVA 00700170988
 e-mail: valsir@valsir.it
 www.valsir.it



valsir[®]
 QUALITY FOR PLUMBING

power transfer

- موجوده صورة التوصيلة
ع القوسه -

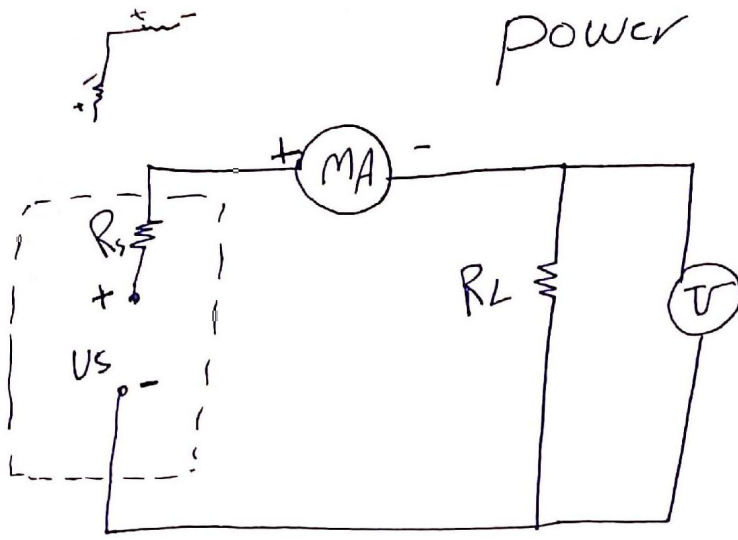


بدي احسب \rightarrow Power desipated in Load Resistance

$$P = I U$$

من خلال الفولتميتر $U_L (V)$ $P_L (mW)$
من خلال الاميتر $I_L (mA)$

$R_L = R_s$ max. power *
When $R_{source} = R_L$

- عند اي R_L اى power

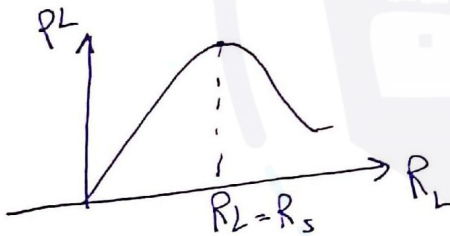

- الجزء العملي *

الان فولت :

resistance / power supply / resistance
source or box /
مرفقه من 20-1000

Ameter / Voltmeter

[1] بوهيك + ال power supply مع ال source resistance

[2] بعدها سالب ال source مع resistance

[3] موجب ال (A) مع القاب ال- ترزمه R_L

[4] سالب ال (A) مع ال - ال power supply

[5] بوهيل - ال Voltmeter مع السلك لكي واطل مع الا شير مع التوصيل فوفه
وار + مع ال R_L فوفه

مسئله
فيعا ايقظان
اصليه R_L

← # مطلوب P_{max} → الاستان

$$P_L = I_L U_L$$

$$U_L = I_L (I_L R_L)$$


$$= I_L^2 R_L$$

$$I_L = \frac{U_s}{R_L + R_s}$$

$$P_L = \left(\frac{U_s}{R_L + R_s} \right)^2 R_L$$
 To find at what value of R_L P_L is max

$$\frac{dP_L}{dR_L} = 0$$
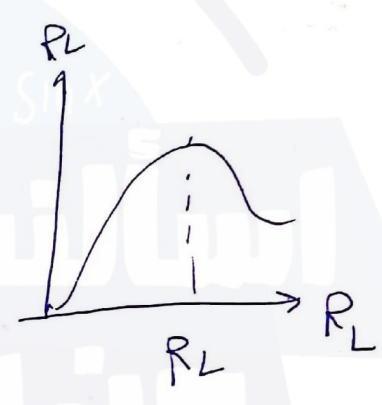
$$\frac{dP_L}{dR_L} = \frac{-U_s^2 (2(R_L + R_s))}{(R_L + R_s)^4}$$



$$U_s^2 (2(R_L + R_s)) = 0$$

$$R_L + R_s = 0$$

$$R_L = R_s$$

$$\frac{dP_L}{dR_L} = \frac{U^2 (R_L (2(R_L + R_s)) - U^2 (R_L + R_s)^2}{(R_L + R_s)^4} = 0$$

$$U^2 R_L (2(R_L + R_s)) = U^2 (R_L + R_s)^2$$

$$2R_L = R_L + R_s$$

$$\therefore R_L = R_s \quad \#$$

EXPERIMENT 4 POWER TRANSFER


- The Power P is defined as the rate at which energy is delivered to the resistor.
(تم تعريف القدرة الكهربائية على أنها معدل انتقال أو مرور الطاقة خلال المقاومة الكهربائية)

$$P = I \Delta V$$

$$\text{And Since } \Delta V = I R$$

$$P = I^2 R = (\Delta V)^2 / R$$

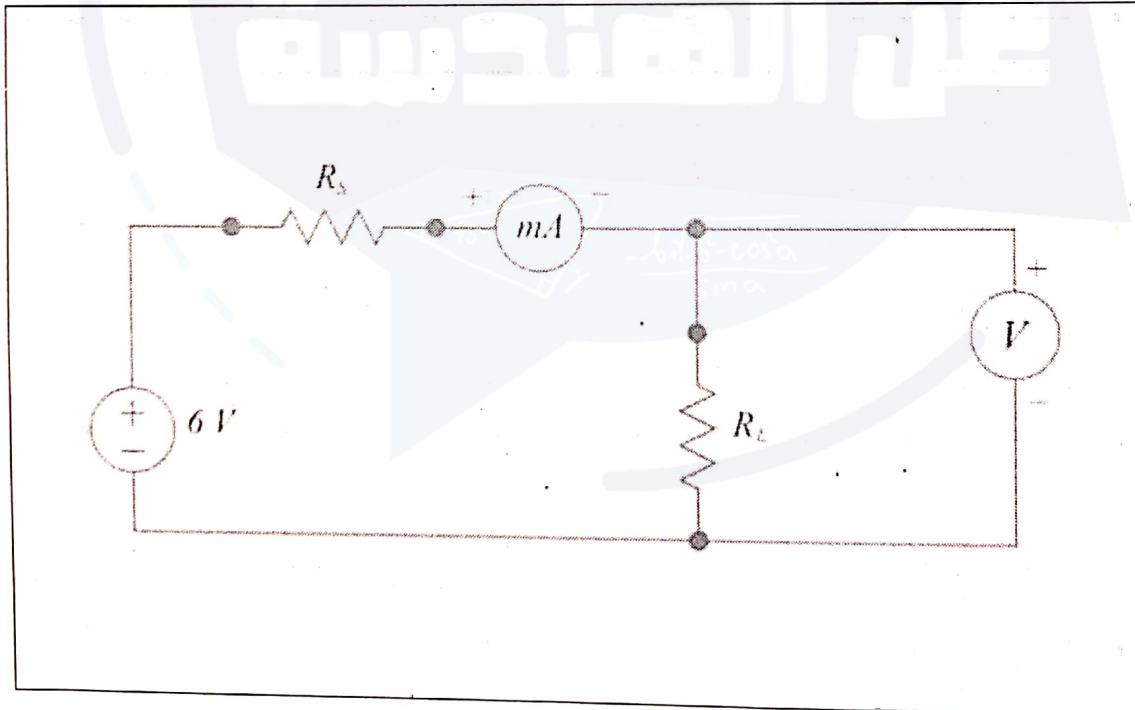- SI units of Power are *Watts* (W):
 - $1 \text{ W} = 1 \text{ A} \times 1 \text{ V}$
 - Therefore, $1 \text{ mW} = 1 \text{ mA} \times 1 \text{ V}$
- In the **Power Transfer** experiment, we will investigate the circuit requirements (Conditions) for the transfer of **Maximum Power**, P_{MAX} , from the power source to the load resistance in a DC circuit.



POWER TRANSFER CIRCUIT CONFIGURATION

- The configuration of this circuit is based on two resistors connected in series.
- These resistors are the Load resistor R_L (الحمل أو العبئ على الدائرة) and the Internal resistor R_S (المقاومة الداخلية لمصدر فرق الجهد أو البطارية).
- Since the power supply is made of matter, there is a resistance to the flow of charge within the power supply (battery). This resistance is termed the Internal resistance R_S .
- The Load resistance or the External Resistance, mostly called the Load Resistance R_L . This R_L might be some electrical device such as a toaster, electric heater, or even a light bulb connected to the power supply.
- The MilliAmmeter will measure the Current flowing through the Load Resistor R_L which is the same current that passes also through the Internal resistor R_S (Series Combination).
- The Voltmeter will measure the Voltage across the Load Resistor R_L Only.
- In today's experiment, we want to:
 - **Build up simple electric circuit** using different **circuit elements** including:
 - **Electric wires** (considered as perfect conductors even though they tend to heat up during the experiment, hence, their power dissipation is ignored).
 - **Power Supply** to supply an electric power to the electrical load or circuit.
 - **Two different Resistors:**
 - External or Load resistance R_L : Resistance Box (30 – 1000 Ω).
 - Internal resistance R_S : (110 Ω).
 - **Voltmeter** (0 – 6 V) to register the potential drop across the load resistance, which is connected in parallel to the load resistance.
 - **Milli Ammeter** (0 – 100 mA) to register the current passing through the circuit, which is usually connected in series with the resistances.
 - **Calculate** the power delivered to the load resistance in this circuit configuration.
 - Plot P_L versus R_L and answer the questions as requested in the report.