

Date: -----

Name:-----

Partner's Name:-----

Registration No:-2'

Registration No:-----

Physics Section:-

Instructor's Name:---

PHYSICS LAB EXPERIMENT 7 : THE RC TIME CONSTANT

1. PURPOSE

To determine the time constant
for an RC-circuit by measuring
the charging current

IV. DATA AND DATA ANALYSIS:

- 1- Enter your data of the **charging current**, the corresponding time and the measured voltage source V_0 in Table 7.1 below:

Plot the charging current as dependent variable versus time as independent variable for case 1. Is the plot linear? What can you say about the shape of your graph?

Not linear (decreasing)

3- From the data of charging current versus time, determine the value of the initial charging current I_0 . This is the value of the current at $t = 0$. Record the value in table 7.1.

case 1 $\rightarrow I_0 = 90 \text{ mA}$
 case 2 $\rightarrow I_0 = 90 \text{ mA}$

4- Plot $\ln(I/I_0)$ as the dependent variable versus time. Here, I is the charging current and I_0 , the initial current determined in step (3) above. Is the plot linear?

yes, linear

5- Draw the straight line that best fits the data and determine the slope of the line. Record the value of the slope in table 7.1.

6- Repeat steps 3,4 and 5 above for the second case.

7- Determine the time constant for each case from the equation:

$$\tau = \frac{-1}{\text{slope}}$$

and record it in table 7.1.

τ_1 (experimentally) = +15 2.5

τ_2 (experimentally) = +25 2.5


8. From the known values of C and R for each case, calculate $\tau_1 = RC_1$ and $\tau_2 = RC_2$ and compare these values with those obtained in step (6).

τ_1 (Calculated) = 11.704 μs

τ_2 (Calculated) = 26.796 μs

9- From the known values of V_o and R, , calculate $I_o = \frac{V_o}{R}$ which is the same for both cases. Compare this value with the one obtained in step (3) above.

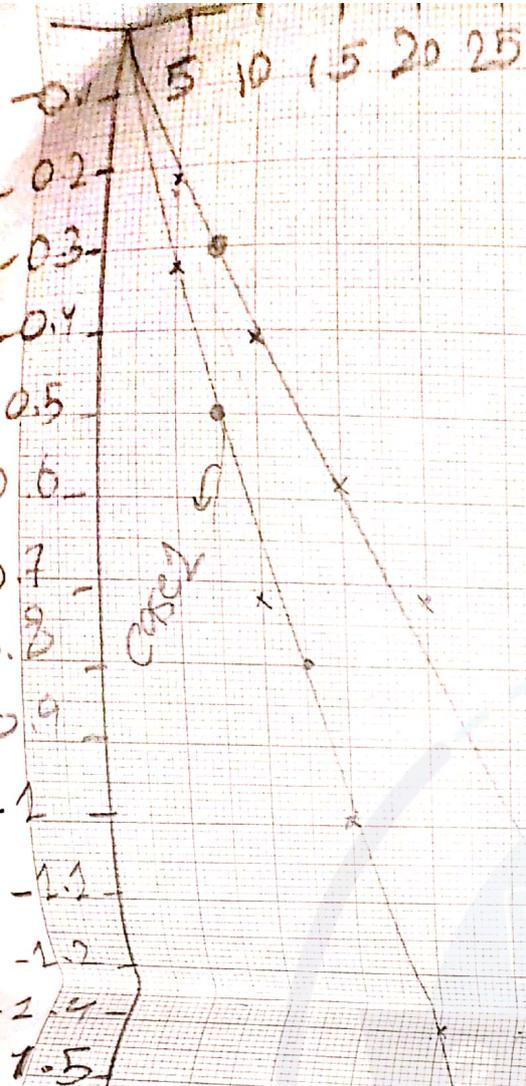I_o (calculated) = $\frac{V_o}{R} = \frac{6V}{(61.6)k\Omega} = 0.097mA$



$$\text{slope}_2 = \frac{-0.5 - 0}{7.5 - 0} = -0.066$$


$$\text{slope}_2 = \frac{-0.3}{7.5}$$

$$\text{slope}_2 = -0.04$$

p.A.
 eriaro, 2
 one (BS) - Italy
 65 877.011
 65 81 268
 170988
 @valsir.it
 ir.it




valsir®

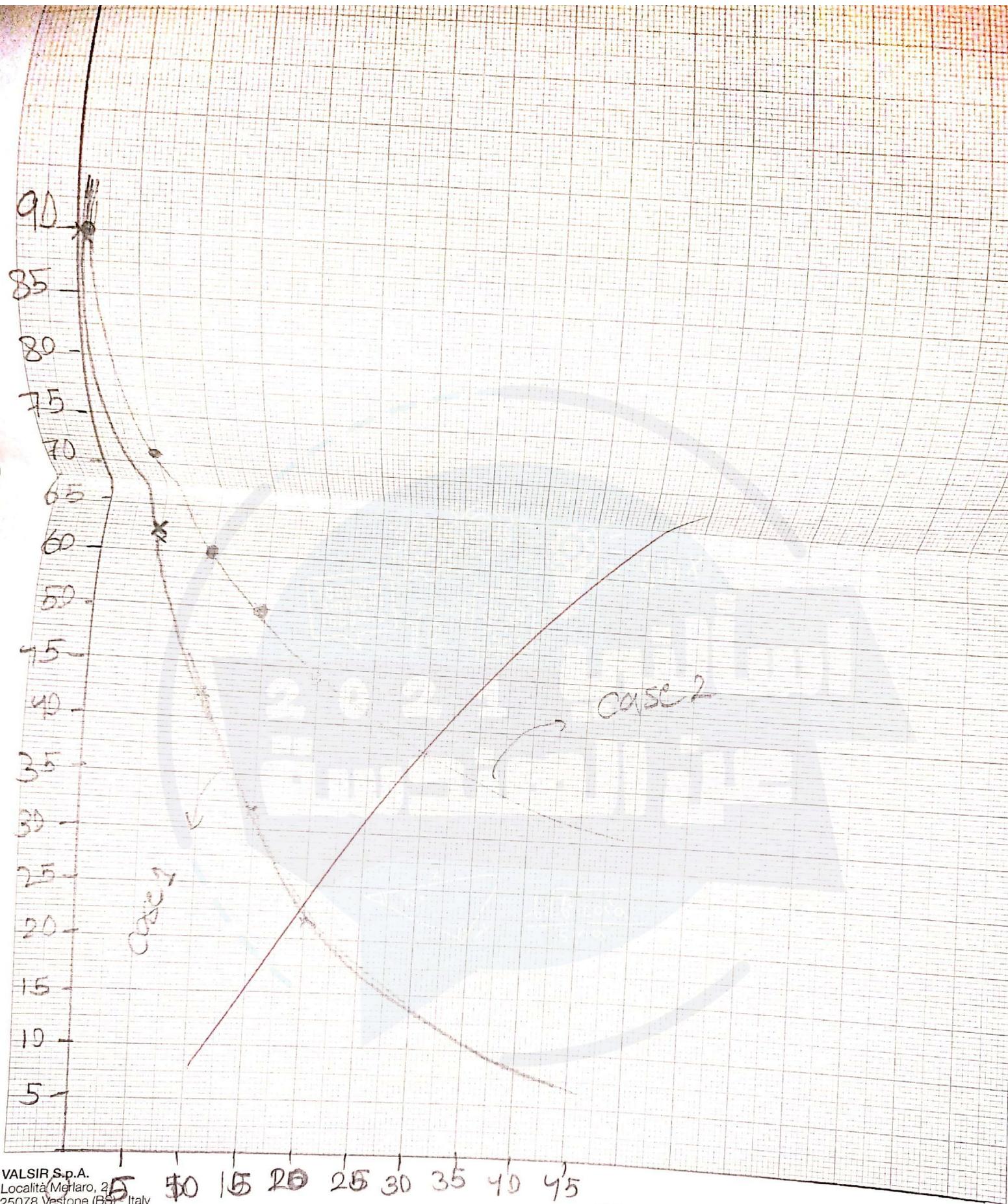

VALSIR S.p.A.
 Località Merlaro, 2
 25078 Vestone (BS) Italy
 Tel. +39 0365 877.011
 Fax +39 0365 81.268
 P.IVA 00700170988
 e-mail: valsir@valsir.it
 www.valsir.it



valsir
 QUALITY FOR PLUMBING

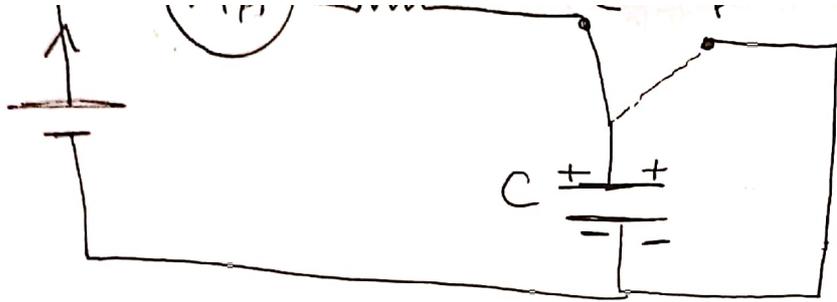

$$C = \frac{Q}{V_c}$$

Farad

مقدار الشحنة
الجهد

بدارة التبريرة ما فيهه أي لشحنة
مقدار الشحنة + = مقدار الشحنة السالبة
ما بين سبي بين الصفين لأن داخله مادة عازلة *
وهادي العملية اسمها

* charging capacitor → switch
ليكون مغلقة

تاو $RC \equiv \tau$

$$V_0 - IR - V_c = 0$$

$$V_0 - IR - \frac{Q}{C} = 0$$

$$V_0 - R \frac{dQ}{dt} - \frac{Q}{C} = 0$$

$$\frac{dQ}{dt} = \frac{V_0 - Q/C}{R}$$

$$\frac{dQ}{V_0 - \frac{Q}{C}} = \frac{dt}{R} \quad * \text{separation variables} *$$

$$u = V_0 - \frac{Q}{C} \rightarrow du = -\frac{1}{C} dQ$$

$$-C \frac{du}{u} = \frac{dt}{R} \rightarrow -C \int_{u_1}^{u_2} \frac{du}{u} = \int_{t_1}^{t_2} \frac{dt}{R}$$

$$\ln u \Big|_{u_1}^{u_2} = \frac{-1}{RC} t \Big|_{t_1}^{t_2}$$

$$\ln u_2 - \ln u_1 = \frac{-t}{RC}$$

$$\ln \frac{u_2}{u_1} = \frac{-t}{RC}$$

if S is closed (at instant closing S at time +)
 $V_c + V_R = 0$
 $V_c = 0$
 $\frac{Q}{C} + IR$


هو لما مشينا
بالكراسة حلنا
سالب جتو حذري
F. f
بغير انحناء
في الجهد
اذا مشينا
في الجهد

$RC \equiv \tau$
time constant
of the RC
circuit

$$Q = CV_0 \left(1 - e^{-\frac{t}{RC}}\right)$$

معادلة الشحنة لتوقيت التبريرة

$$Q = CV_0(1 - e^{-t/\tau})$$

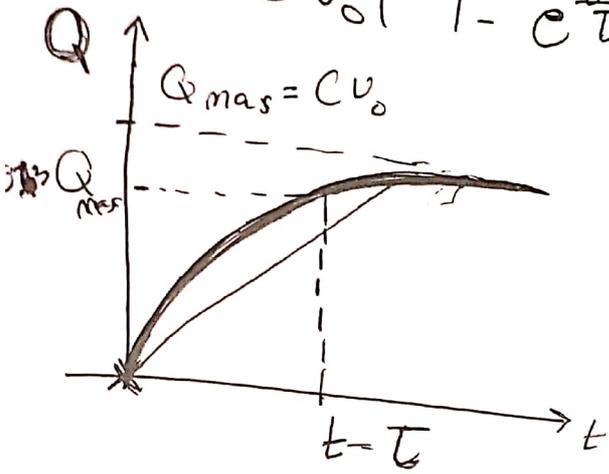

بعد زمن طويل من اغلاق السوييت
 When $t \gg \tau$
 $0 = CV_0(e^{-t/\tau})$ ← بيتر

∴ $Q = CV_0$
 * رصده لـ Q_{max} التي يتجمع مع
 اللصينة تجت المراسية

at $t = \tau$

$$Q|_{t=\tau} = Q_{max}(1 - e^{-1})$$

$$Q|_{t=\tau} = 0.63 Q_{max}$$

بعد زمن τ ال capacitor
 جمع Q_{max} 0.63

at $t = 2\tau$

$$Q|_{t=2\tau} = Q_{max}(1 - e^{-2})$$

$$Q|_{t=2\tau} = 0.84 Q_{max}$$

* مقدار ال τ يحد سرعة شحن ال capacitor
 كلما زادت τ يزيد امدد ازمجة الازمة لشحن ال capacitor
 "السبح ابطء" *

$$I = \frac{dQ}{dt}$$


$$I = \frac{CV_0}{\tau} e^{-t/\tau}$$

$$= \frac{QV_0}{RC} e^{-t/\tau}$$

$$I = \frac{V_0}{R} e^{-t/\tau}$$

$I \rightarrow$ مع زيادة t
 يتناقص

$$I|_{t=\tau} = \frac{V_0}{R} \cdot e^{-1} = 0.37 I_0$$

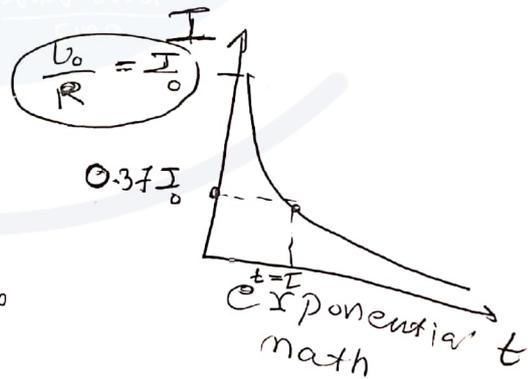

يصل current 0
 بعد زمن طويل
 $R > C \rightarrow$ يزيد τ
 يزيد

$$V_C + V_R = 0$$

$$V_C = 0$$



time +)

$$Q = CV_0 (1 - e^{-t/\tau})$$

$$I = I_0 e^{-t/\tau}$$

$$\ln\left(\frac{I}{I_0}\right) = \frac{1}{\tau} t$$

↘ slope

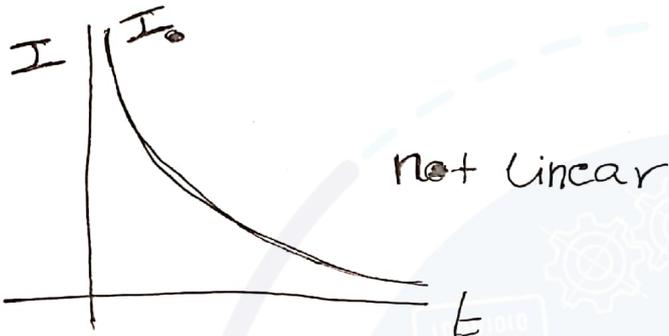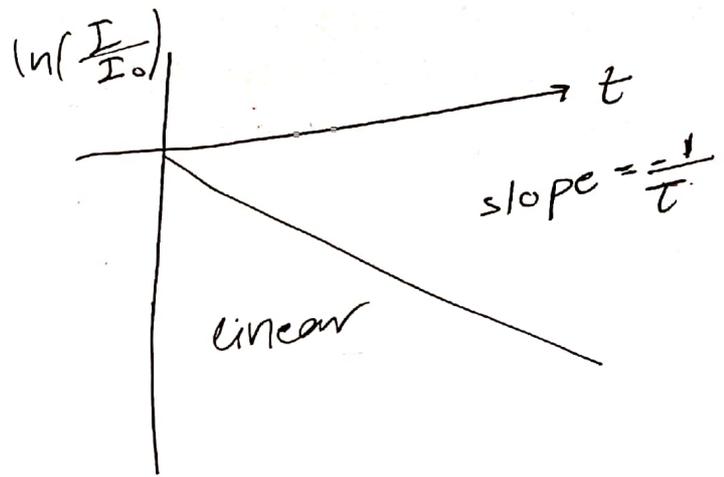

① $I_0 = \frac{\mathcal{E}}{R}$
 $q = 0$
 $I_0 = I_{\text{max}}, I_0$, initial current

② for time t →


$$q(t) = \mathcal{E}C(1 - e^{-t/RC}) \rightarrow \text{بعد زمن}$$

$$i(t) = \frac{\mathcal{E}}{R} e^{-t/RC} \rightarrow \text{بعد زمن}$$

عملية (A)
التفريغ

③ for long time $t \rightarrow$
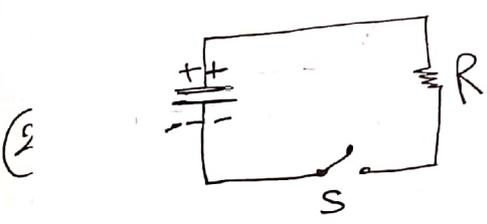
$$q_{\text{max}} = q_{\text{final}} = \mathcal{E}C \approx CV_0$$



1) S is open

$$q_0 = \mathcal{E}C = CV_0$$

$$i_0 = \frac{\mathcal{E}}{R} = \frac{V_0}{R}$$

عملية (B)
التفريغ

2) S is closed (at instant closing S at time t)

$$V_C + V_R = 0$$


$$\mathcal{E} - \Delta V = 0$$

$$\Delta t \rightarrow \frac{q}{C} + iR = 0$$


$$i(t) = \left(\frac{\mathcal{E}}{R}\right) e^{-\frac{t}{T}} \quad \text{--- (1)}$$

$$q(t) = (q_0) e^{-\frac{t}{T}} \quad \text{--- (2)}$$

$\mathcal{E}C = CV_0$

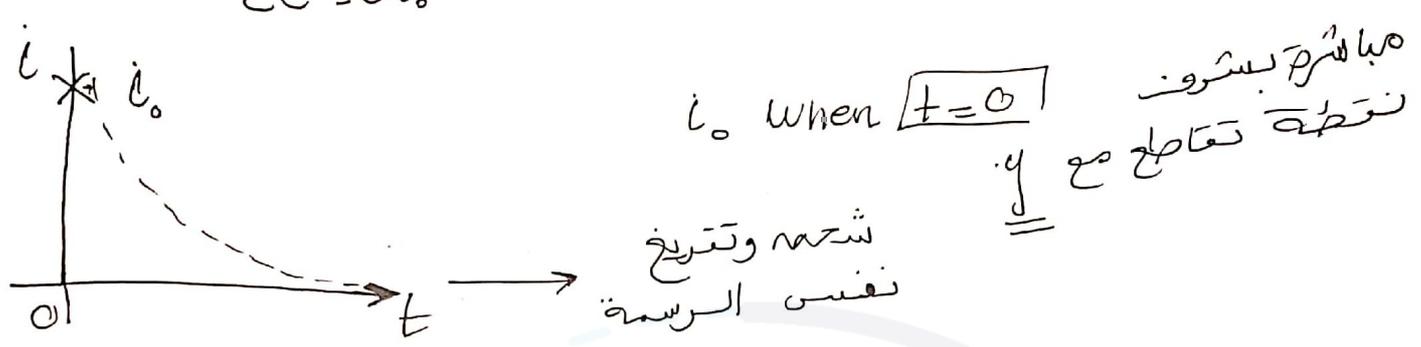

استاذنا
2021
عن العزمية

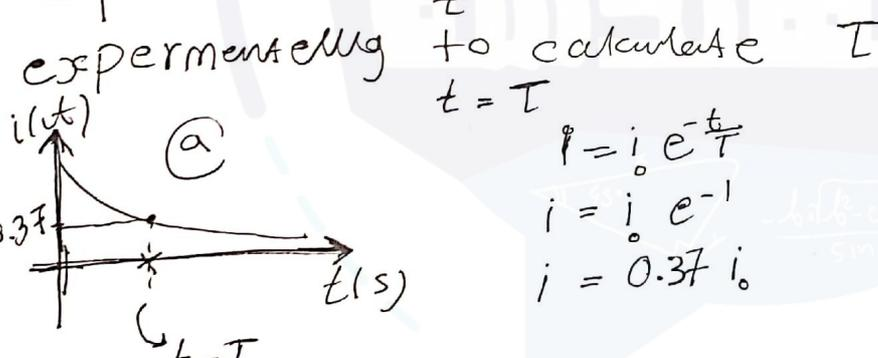

$$i = i_0 e^{-\frac{t}{T}}$$


$$i = i_0 e^{-1}$$

$$i = 0.37 i_0$$

مخزن
إيجاد T

(b) $T = RC$

\downarrow
 $\frac{V}{I}$

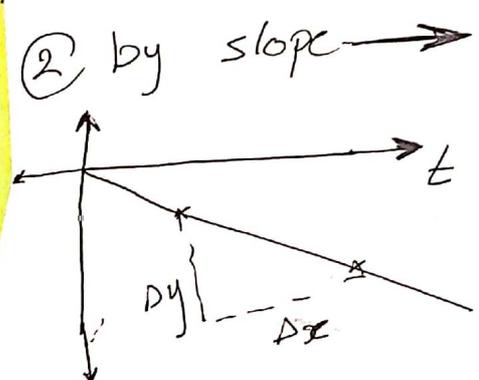

نأخذ ln الطرفين

$$\ln\left(\frac{i}{i_0}\right) = -\frac{t}{T}$$


$$\ln\left(\frac{i}{i_0}\right) = -\frac{t}{T}$$

$$\text{slope} = \frac{\Delta \ln\left(\frac{i}{i_0}\right)}{\Delta t}$$

(c) $T = \frac{1}{|\text{slope}|}$

Multimeter & read deflection = i

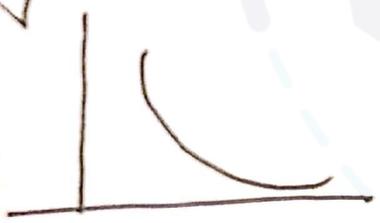
Which of the following represent discharge process.




a ✓



b

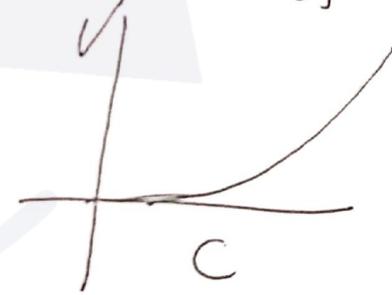

c

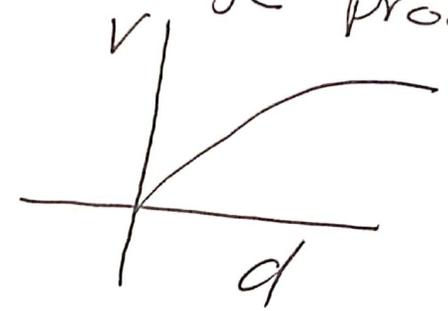

d

in circuit shown time constant ? (in sec)

$$= RC$$

$$= 20 \times 10^{-6} \times 7 \times 10^6$$

$$\tau = 140 \text{ sec}$$



10 MF

توکل ال C هو مجموع
طیعی