

LAB REPORT FOR EXPERIMENT 6

Name:-----

(9.5)

Partner's Name:-----

Registration No:-----

3

Registration No:-----

Physics Section:-----

Instructor's Name:-----

PHYSICS LAB EXPERIMENT 6: THE POTENTIOMETER

1. PURPOSE:

We will use the potentiometer to
measures an known electromotive
force (emf) or an known potential
difference.

II. DATA AND DATA ANALYSIS :

A. Calibration of the Potentiometer

1- Record your measurements of the reading V_x of the voltmeter at any point on the wire and the corresponding distance L_x in Table (6.1) below:

Table (6.1)

Reading	V_x (V)	L_x (cm)
1	0.2	15
2	0.8	30
3	1.2	45
4	1.6	60
5	2	75
6	2.5	90

Plot a graph of V_x versus L_x . State your conclusion.

it is direct linear relationship

3- If the wire is uniform derive a simple relation between the voltmeter reading V_x at any point on the wire and the corresponding distance L_x .

$$R = \left(\frac{\rho}{A}\right) L, \quad R \propto L$$

$$V_x = \left[\frac{I \rho}{A}\right] L_x$$

$$V_x = \text{slope} \times L_x$$

B. Measurement of an Unknown EMF

1- Calculate and record \bar{L}_x , the average value of L_x .

Trial	L_x (cm)
1	58
2	
3	
$\bar{L}_x =$	cm

2- Use your graph of part A to find the value of E_x corresponding to \bar{L}_x .

$$E_x = \frac{0.6}{22.5} (58) = 1.546 \text{ volt}$$

3- What is the current flowing through E_x when pointer touches the potentiometer wire at the balance point?

~~$I=0$, because $V=0$ (balance point)~~


4- What happens to the balance point when a small resistor is connected in series between E_x and the galvanometer? Explain the result you observe.

~~Nothing happen because $I=0$
so E_x is the source~~

data / date

titolo / title

V (Volt)

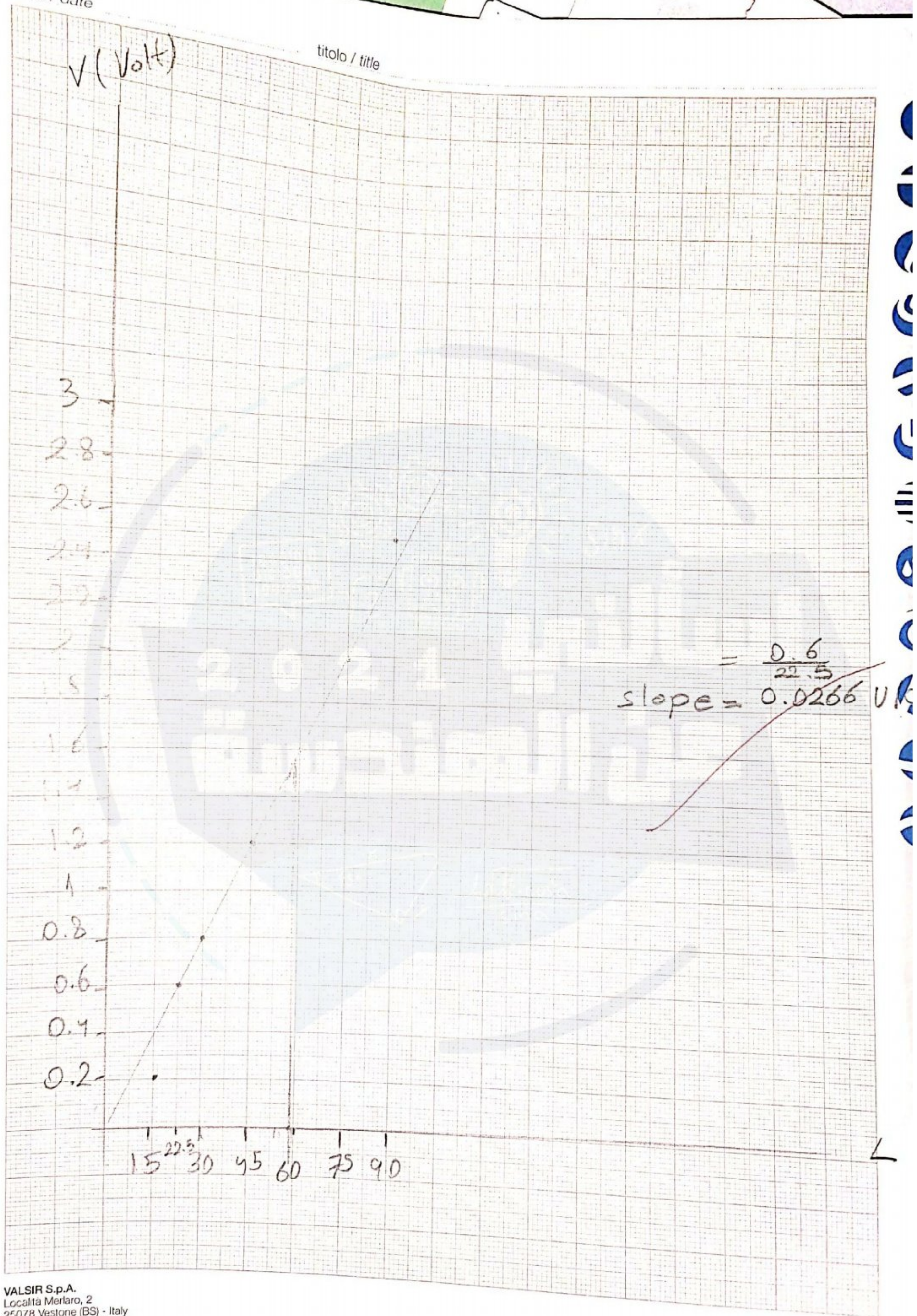


VALSIR S.p.A.
 Località Merlaro, 2
 25078 Vestone (BS) - Italy
 Tel. +39 0365 877.011
 Fax +39 0365 81.268
 P.IVA 00700170988
 e-mail: valsir@valsir.it
 www.valsir.it



valsir®

EXPERIMENT 6
THE POTENTIOMETER

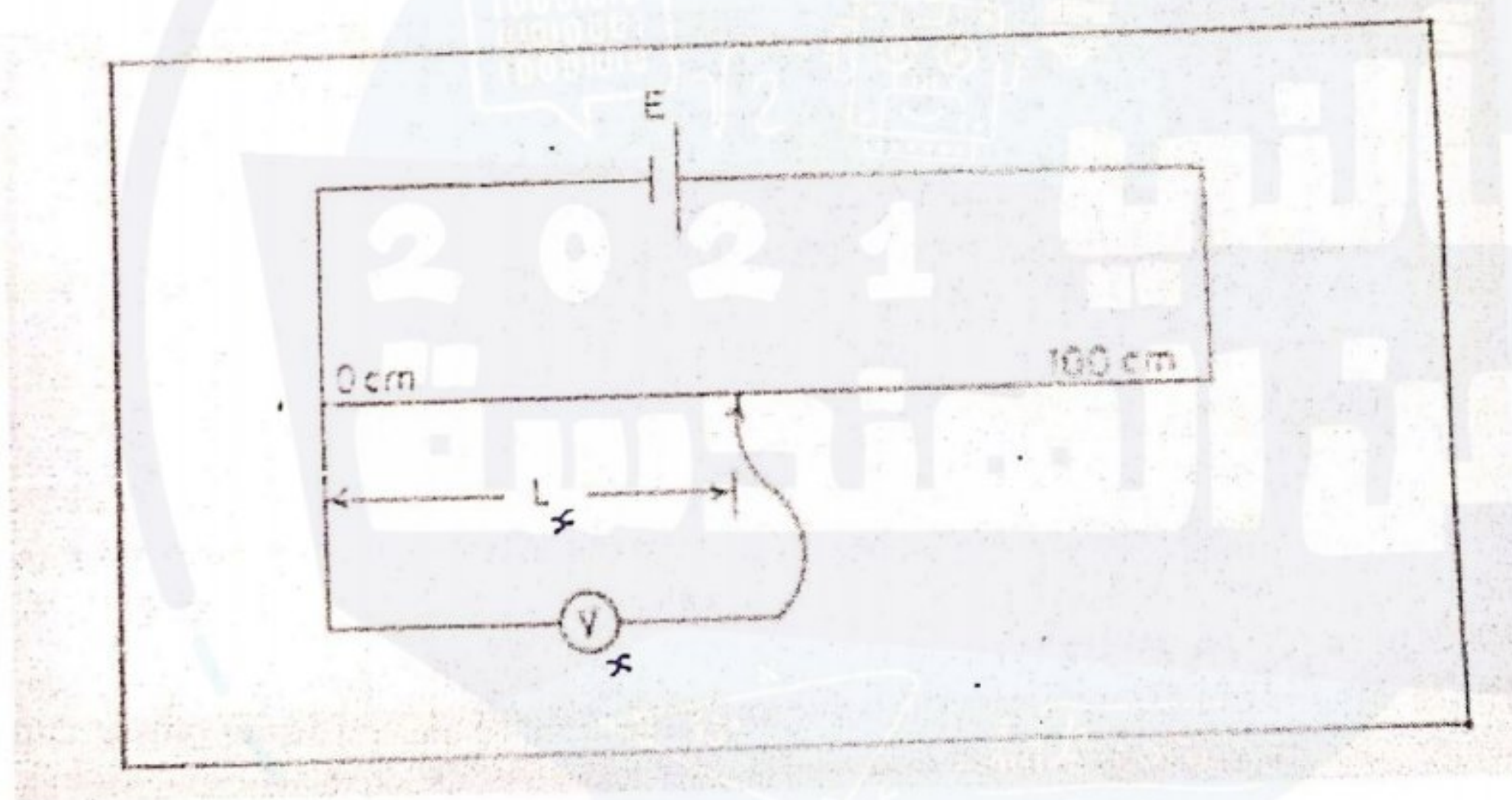
- In the Potentiometer experiment, the circuit configuration will allow for the determination of an Unknown Electromotive Force (emf) E_X or an Unknown Potential Difference V_X by comparison with the emf of a standard cell E_B .
- Initially, the Potentiometer will be Calibrated using a Voltmeter.
- Then by using the Calibration Curve, the unknown emf E_X is determined.



~~1/5~~ 2 parts

CALIBRATION OF THE POTENTIOMETER FIG 6.1

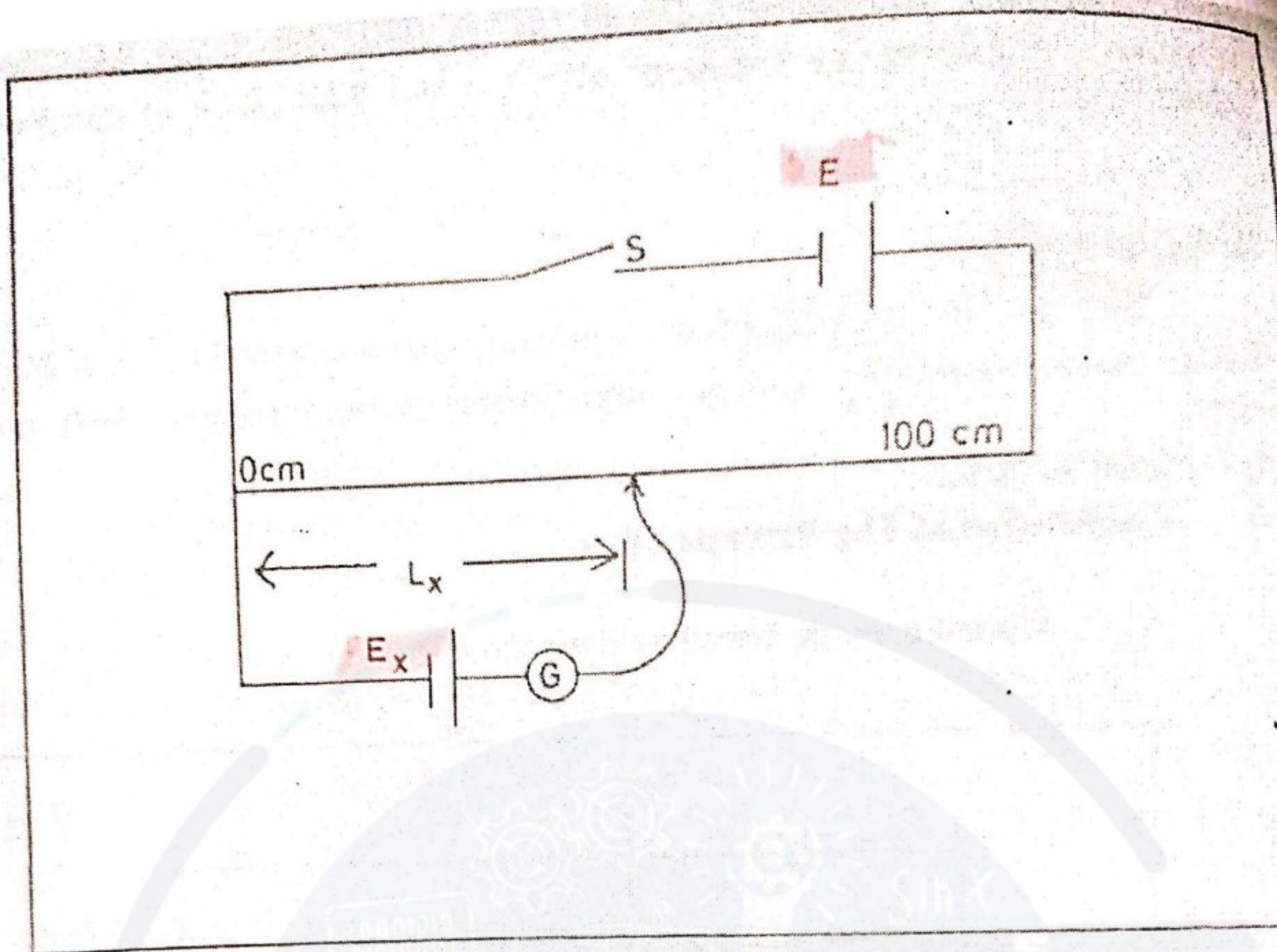- Table 6.1 will be filled by the measured values of V_X versus L_X for the Calibration Curve which is a graph of V_X (as dependent variable) versus L_X .
(Remember that the Potentiometer wire will heat up if measurements took longer time).
- Later, another circuit configuration will be set up to allow the use of the calibration curve for the determination of the unknown emf E_X .



Scanned with CamScanner

MEASUREMENT OF AN UNKNOWN EMF, FIG 6.2

- Using the Galvanometer will allow to locate the Balance Point P at which L_X is recorded (This should be done three times and average value is calculated $\overline{L_X}$.
- Using the Calibration Curve, the value of E_X corresponding to $\overline{L_X}$ will be found.

THE POTENTIOMETER CONFIGURATION



- In today's experiment, we want to:
 - Build up simple electric circuit using different circuit elements including:
 - Electric wires (considered as perfect conductors even though they tend to heat up during the experiment, hence, their power dissipation is ignored).
 - DC Power Supply (3.0 Volts).
 - Two different Resistors:
 - Meter Bridge (wire resistance).
 - Resistance (5 – 10 Ω).
 - Voltmeter to register the voltage correspondance of the current passing through the wire resistance.
 - Galvanometer to register the balance point.
 - Unknown emf E_X .
 - Plotting a Calibration Curve
 - Calculating the average value of $\overline{L_X}$.
 - Determining the unknown emf E_X .

الجزء الثاني
 ↓
 Voltmeter
 الثاني
 Galvanometer

The Potentiometer

تجربة هدفها قياس القوة الدافعة لمصدر قوة دافعة معلومة

part 1: Calibration of the potentiometer

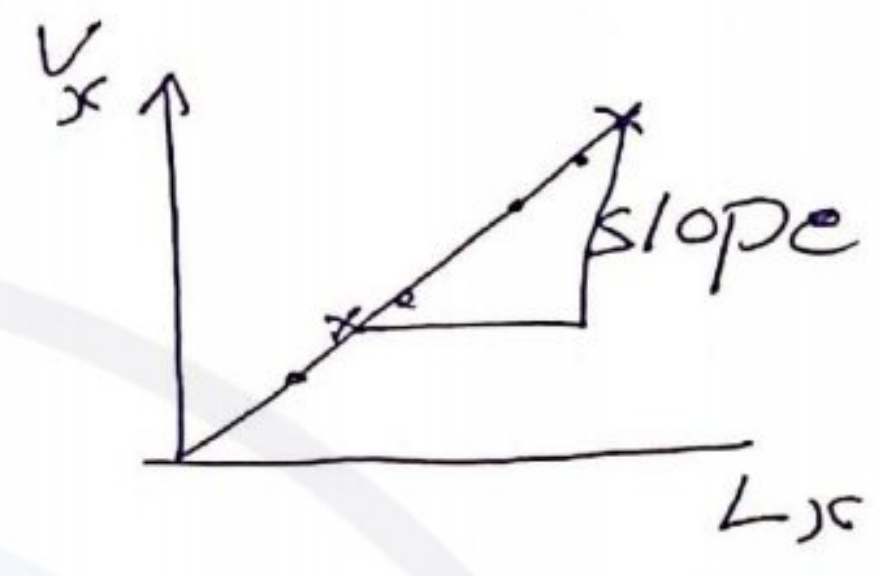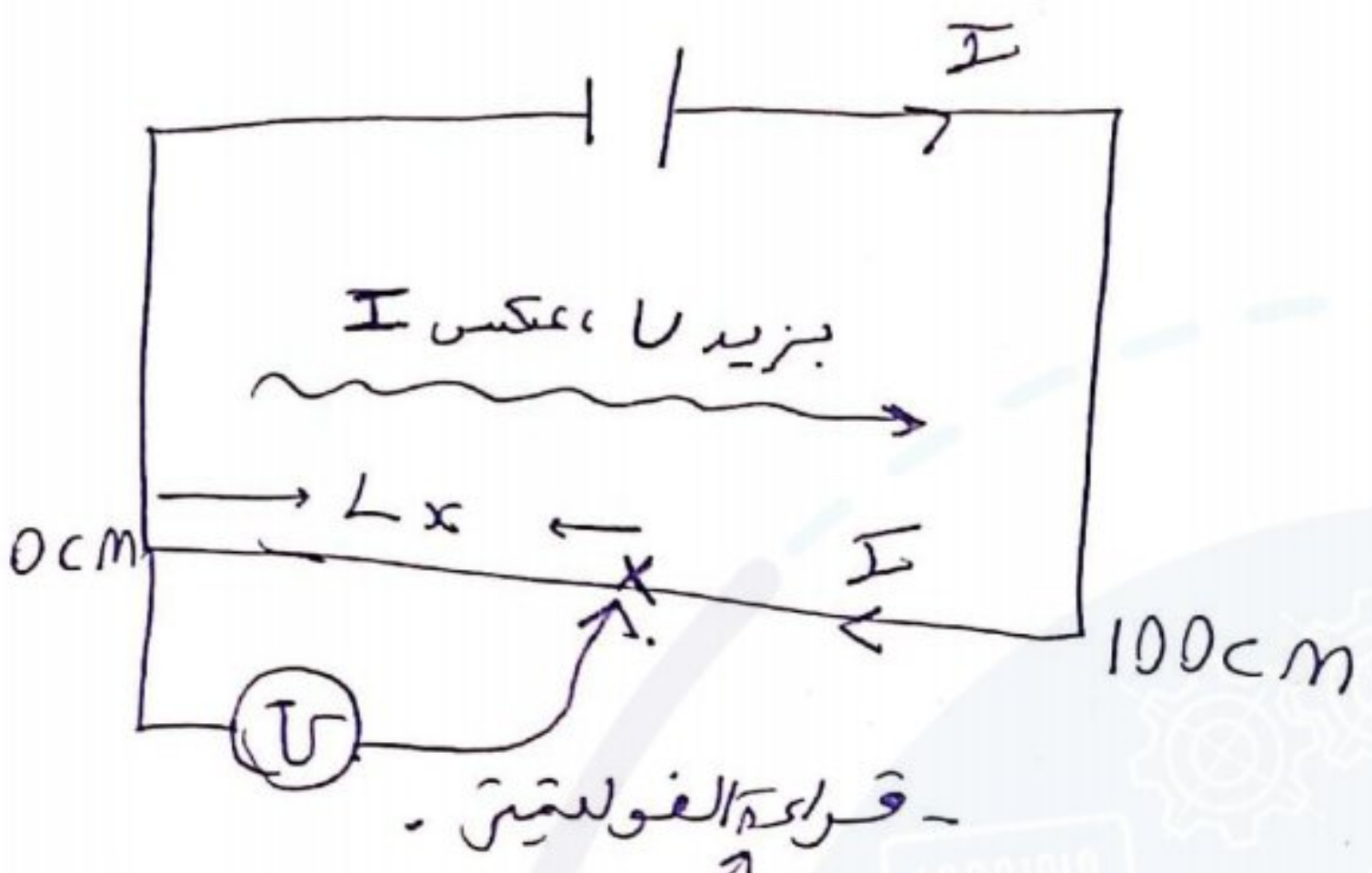

بتوصيل فرق الجهد بدلالة L_x

$L_x (cm)$ $V_x (Volt)$ $V_x = (slope) L_x$

بوصل الـ sliding contact مع Voltmeter يلمس فيها السلك العزلي ، فيقيس فرق الجهد

$$R = \frac{L_x \rho}{A}$$

كل ما زاد طول تزييد الـ R

$$V_x = IR$$

تعتمد على L

$$\therefore V_x = I \left(\frac{\rho L_x}{A} \right)$$

ثوابت


slope

$$\therefore V_x \propto L_x$$

ليس اجب slope لقيتر احسب الـ لا عند L_x مش موجود على الطول الاناسي "غير مقاس بعين"

بزيادة فرق الجهد اذا مشيت بحس الـ current

Part 2: Finding the known emf

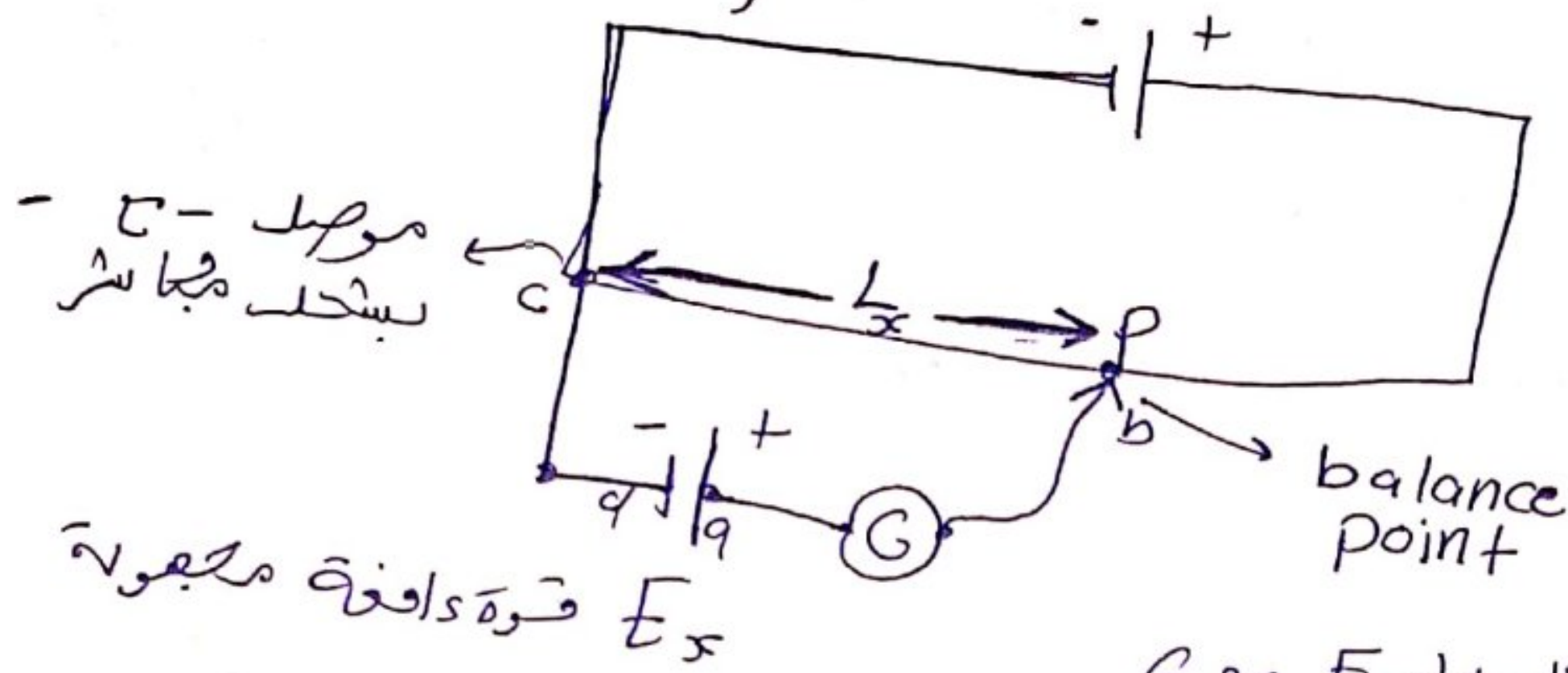

Balance point

هي

$$0 = G$$

وبحث عن النقطة التي $G = 0$ عن طريق التحريك من جهة إلى جهة أخرى حتى $G = 0$ نفس الجهد

$$dq = cb$$

$$E_x = (\text{slope}) L_x$$

Part 1: العملي

الموجب لا power مع ال 100 cm والسالب مع 0cm للسلك
 سالب ال Volt meter مع ال zero والموجب مع ال pointer
 sliding contact

بعد هابتقرأ المسافة وبقراء ال V
 ونحرك وباخذ قيم

Part 2

بدا ال Voltmeter عنيفاً قوة دافعة
 مع ال zero الي موصل مع السالب
 بطارية سالب
 والموجب للبطارية مع سالب
 ال Voltmeter والموجب مع ال pointer ويحرك Balance point
 ال Voltmeter لا يعرف لليساير، جهة ال 100 للـ