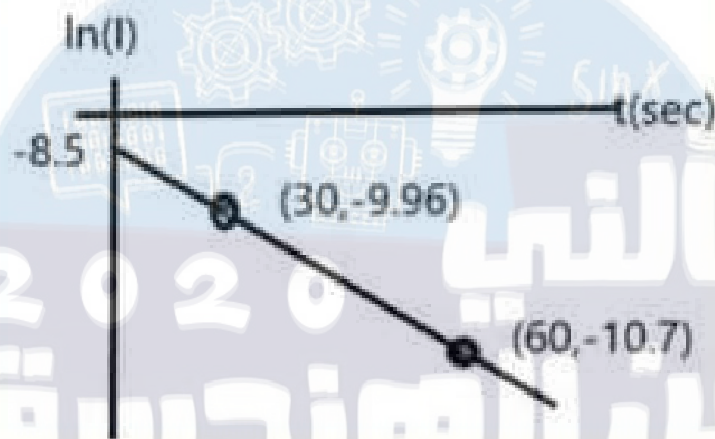


The figure below represents the charging process for a capacitor of value C connected to a power supply ($V = 5\text{ Volt}$) across resistance R .


The approximate values of R and C respectively are



Select one:

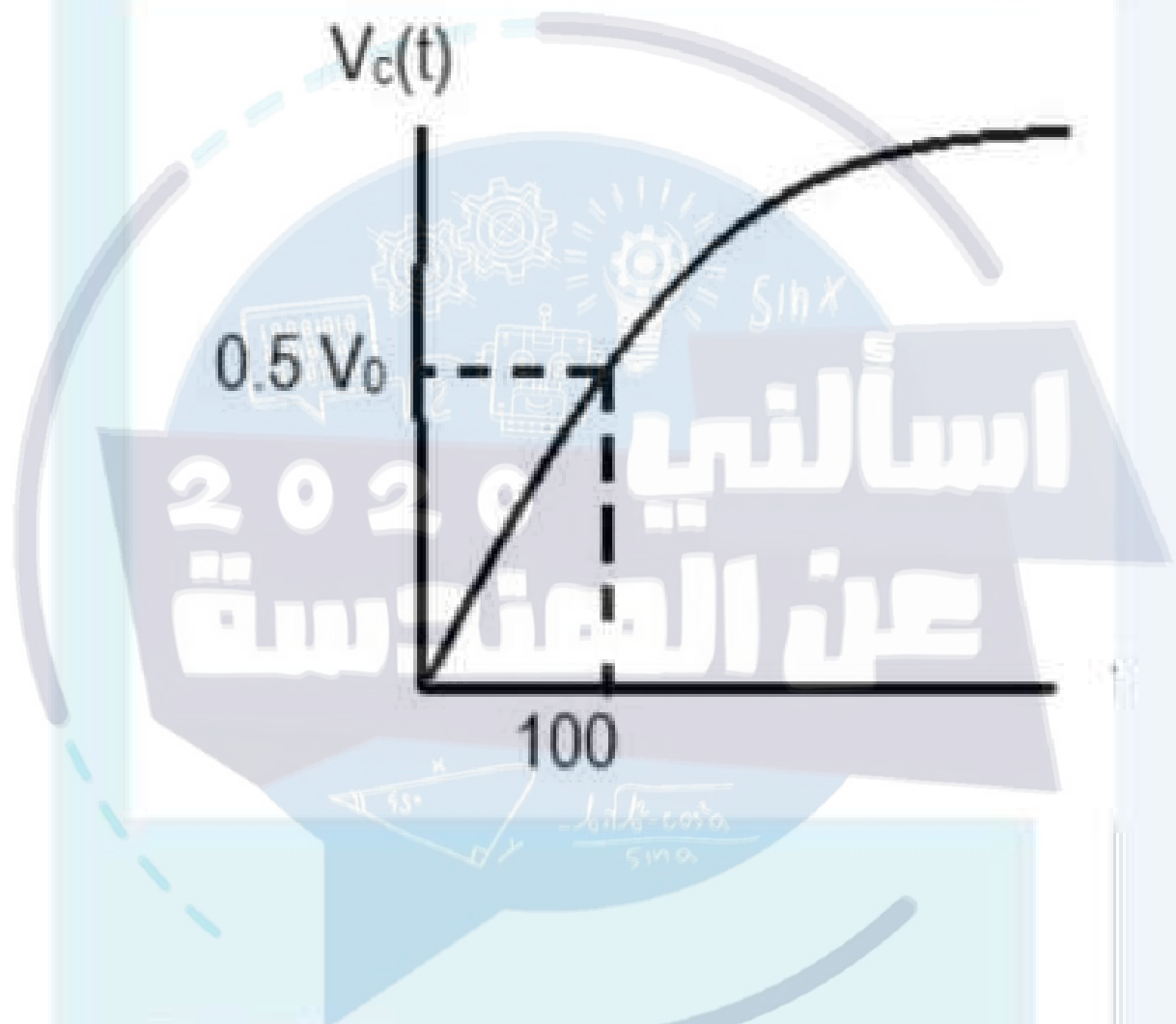- a.
50K Ω , 800 μF
- b.
20K Ω , 16 μF
- c.
25K Ω , 1600 μF
- d.
10K Ω , 80 μF

Depending on the graph of V_c versus t for the charging process in RC circuit, the time constant τ (in second) is:




Select one:

- a. 145
- b. 187.55
- c. 158.7
- d. 173.12

In the RC-Time Constant Experiment, if the capacitance is $80 \mu\text{F}$ and the resistance is $2.0 \text{ k}\Omega$, then the time constant (in ms) of the circuit is:

- 160
- 40
- 52
- 18
- 14

اسألني
2020
عن المهندسة

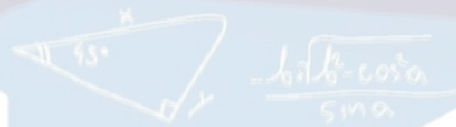

The time constant τ of RC circuit depends on:

Select one:

- a. resistance
- b. current
- c. inductance
- d. both a and c

In a RC circuit with power supply with an emf of 20 V, capacitance $3 \mu\text{F}$, and resistance 1000Ω , the slope (in units of C/s) of the curve of Q (the charge on the capacitor) vs t (the time elapsed after starting the charging) at $t = 0$ s is:

- a. 0.2
- b. -0.2
- c. 0
- d. 0.02
- e. -0.02

اسألني
2020
عن الهندسة

Time left 0:10:46

In a RC circuit starting from zero capacitor charge, during charging:

- a. The potential across the capacitor is decreasing and its charge is increasing.
- b. The magnitude of the potential difference across the capacitor is increasing but is decreasing across the resistor.
- c. The current in the circuit is decreasing but the potential difference across the capacitor is constant.
- d. The time it takes to charge the capacitor to half its maximum charge is half the time needed to fully charge the capacitor.
- e. The current decreases with time linearly.

Next page

Question 10

Not yet answered

Marked out of 4.00

Flag question

In a RC circuit with power supply with an emf of 10 V, capacitance $5 \mu\text{F}$, and resistance 1000Ω , the slope (in units of C/s) of the curve of Q (the charge on the capacitor) vs t (the time elapsed after starting the charging) at $t = 0$ s is:

- a. 0
- b. -0.1
- c. -0.01
- d. 0.1
- e. 0.01

[Clear my choice](#)

Question 13

Not yet
answeredMarked out of
4.00Flag
question

In a RC circuit starting from zero capacitor charge, during charging:

- a. The time it takes to charge the capacitor to half its maximum charge is half the time needed to fully charge the capacitor.
- b. The potential difference across the capacitor is decreasing and its charge is increasing with time.
- c. The current in the resistor decreases with time linearly.
- d. The current in the resistor is decreasing but the potential difference across the capacitor is constant.
- e. The the current in the resistor is decreasing and the magnitude of the potential difference across the capacitor is increasing.

[Clear my choice](#)